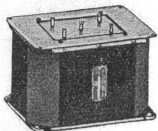




AND NOW THE NEWEST 1935 DEVELOPMENT FROM  
THE UTC ENGINEERING LABORATORIES . . . .

## THE VARITONE\* AUDIO TRANSFORMER

A universal audio input transformer giving continuously variable low end, high end, or low and high end equalization.




VT-1—Designed to work from a single plate or low impedance broadcast microphone line to one or two grids.

List price \$8.50—net to dealers \$5.20  
Affords 15 DB controllable correction of low frequency response, high frequency response, or simultaneous correction of low and high frequency response.

The VARITONE is an essential component for high fidelity theatre and PA amplifiers. Manufacturers of such equipment are invited to write us regarding the application of the VARITONE to their equipment.


\*PATENT APPLIED FOR

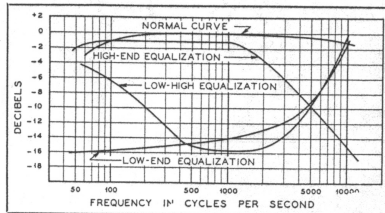

Typical Components for Use in a Popular Priced High Fidelity Receiver Amplifier  
.. Using the VARITONE as an Input Source.

	List Price	Net Price
PA-238 From two triode plates to 45 A prime grids.....	\$ 6.00	\$ 3.60
PA-245 From two A prime 45 plates to Broadcast and Voice coil lines	7.00	4.20
PA- 22 45 A prime plate and filament supply transformer.....	10.00	6.00
PA- 40 A prime input choke.....	4.50	2.70
PA- 44 Output smoothing choke.....	4.50	2.70
	\$32.00	\$19.20

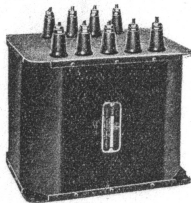What This  
Universal  
Modulation  
Choke  
Will Do:



It is tapped so that it can be used as an autotransformer coupler from Class B to Class C stages; various impedance taps are available so that each choke will readily accommodate push pull Class A-Prime or Class B Modulators, single ended Class A Modulator with the DC add-on, or single ended Class A Modulator with the DC bucking.

The chokes are huskily constructed and air gaps are arranged to take care of the maximum DC currents.

Broadcast and phone men who want an output audio unit that will match all possible tube impedance combinations to the RF Stage cannot afford to be without the new UTC Universal Modulation Output Chokes.

TYPE		LIST PRICE	NET TO HAMS
HUC-20	Will handle 20 watts audio power. Can be used with class B 46's, 59's, 63, 6A6, 79, etc., or class A 2A3's, class A prime 42's, 45's, etc.	\$7.00	\$4.20
HUC-50	Will handle 50 watts audio power. Suitable for use with class B 210's, 801's, 820's, 841's, push pull parallel 45's or 59's, push pull parallel 45's A prime, push pull parallel 2A3's.	\$12.50	\$7.50
HUC-100	Will handle 100 watts audio power. Suitable for use with class B 800's, 211E's, A prime 28's, 845's, etc.	\$20.00	\$12.00
HUC-200	Will handle 200 watts audio power. Suitable for use with class B 203's, 830B's, HK-354's, single EIMAC 150T, push pull parallel 845's, prime, etc.	\$32.50	\$19.50
HUC-500	Will handle 500 watts audio power. Suitable for use with class B 204's, HK354's, EIMAC 150T's, A prime 212D's, A prime 849's, etc.	\$80.00	\$48.00

Complete circuit matching dots furnished with each unit.

## UNITED TRANSFORMER CORP.

264-266 CANAL STREET

Export Division, 15 Laight St., New York, N. Y.

NEW YORK, N. Y.

Exclusive UTC distributors carrying a complete stock of UTC products.

Goldhamer's, Inc.	610 Haron Road, Cleveland, Ohio	Camerasdo Company.....	603 Grant Street, Pittsburg, Pa.
Wholesale Radio Service Co., Inc.	109 Sixth Ave., New York, N. Y.	W. H. Edwards & Co.	32 Brax, Providence, R. I.
Wholesale Radio Service Co., Inc.	219 Central Ave., Newark, N. J.	SEATTLE, WASH.—Seattle Radio Supply Inc.	2319 Second Ave.
Wholesale Radio Service, Inc.	430 W. Peachtree St. N. W., Atlanta, Ga.	Portland Radio Supply Co.	1300 W. Burnside, Portland, Ore.
Sun Radio	227 Fulton Street, New York, N. Y.	Spokane Radio Co., Inc.	611 First Ave., Spokane, Wash.
Gross Radio, Inc.	51 Vesey Street, New York City	San Francisco Radio Exchange	1284 Market St., San Francisco, Calif.
Leeds	45 Vesey Street, New York City		
William Gram	1444 Sheridan St., Lansing, Mich.	SOUTHERN CALIFORNIA	
Mohawk Electric Co.	1335 State St., Schenectady, N. Y.	Pacific Radio Exchange Inc.	729 S. Main St., Los Angeles
Walter Ashe	1106 Pine St., St. Louis, Mo.	Radio Supply Co.	912-14 S. Broadway, Los Angeles
Radio Shack	46 Brattle St., Boston, Mass.	Coast Electric Co.	741 G. St., San Diego
Nutter & Cross	990 Milk St., Boston, Mass.	Prest & Dean Radio Co.	400 American Avenue, Long Beach
Radio Service Lab. of N. H.	1008 Elm St., Manchester, New Hampshire	Radio Television Supply Co.	1701 S. Grand Ave., Los Angeles, Calif.
Hatry & Young	203 Ann St., Hartford, Conn.	Radio Specialties Co.	1816 West 8th St., Los Angeles, Calif.

OHM'S LAW

$$E = I \times R$$

$$R = \frac{E}{I}$$

$$I = \frac{E}{R}$$

CONDENSERS IN SERIES

$$C_{TOTAL} = \frac{C_1 \times C_2}{C_1 + C_2}$$

RESISTANCES IN PARALLEL

$$R_{TOTAL} = \frac{R_1 \times R_2}{R_1 + R_2}$$

25c [30c in Canada]

JANUARY, 1935

\$3.00 PER YEAR BY SUBSCRIPTION

# RADIO

ESTABLISHED 1917

SHORT-WAVE AND EXPERIMENTAL

- IN THIS ISSUE -

The First Practical 5-Meter Superheterodyne

A Link-Coupled High-Frequency Receiver


Complete Data on New RCA-802 Pentode

High-Fidelity Audio Amplifier Problems


Hum-Free Pre-Amplifiers for Amateur Phone

Mercury Vapor Rectifier Tube Considerations


BOTTOM VIEWS OF SOCKETS

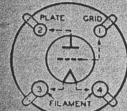

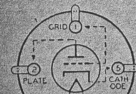
4-PRONG SOCKET  
50-201-A, 45, 210, 30, 31, ETC.




5-PRONG SOCKET  
56-46-47-76-27-57

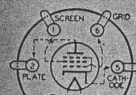


6-PRONG SOCKET  
2A5-41-42-43

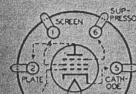

6-PRONG SOCKET  
57-58-606-606-77-78

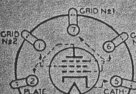


7-PRONG SOCKET 59

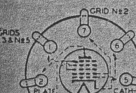

7-PRONG SOCKET  
2A7-6A7



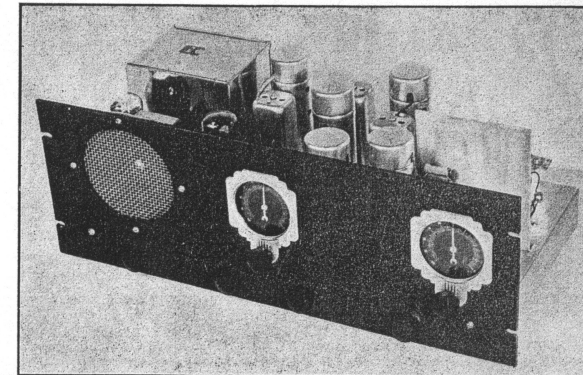Frank C. Jones'  
5-Meter  
Superheterodyne  
—The First  
Workable  
Receiver  
of Its Kind.  
See Page 8.



FEATURE ARTICLES BY...

CLAYTON F. BANE  
J. N. A. HAWKINS

FRANK C. JONES  
FRANK LESTER

COL. C. FOSTER  
I. A. MITCHEL'

# "WE USE 'EM AND LIKE 'EM"

## Sylvania GRAPHITE ANODES

**RADIO STATION WFBE, INC.**  
MEMBER STATION - THE AMERICAN BROADCASTING SYSTEM  
STUDIO AND EXECUTIVE OFFICES  
HOTEL MAYTON  
CINCINNATI, OHIO  
24 November, 1934.

Patented 2188  
Patented 2188

Hygrade Sylvania Corp'n.,  
Electronics Department,  
Clifton, N. J.  
Attn: Mr. C. A. Rice, Sales Mgr.

Dear sir:

We purchased and installed five (5) Sylvania Type 212-D transmitting tubes of a April, 1934 one being used in the modulator stage of our transmitter, the other four being used in our line amplifier push-pull stage, with two tubes in parallel on each leg of the circuit.

These were in continuous use for 17 hours daily from that date (3 April, 1934) until the present time when they were replaced by another set.

This replacement was not absolutely necessary, inasmuch as the old set, when tested, still proved up to virtually the same standard values (plate current, etc.) as previous when they were installed in the set. As a matter of fact, they checked almost as good as the new set for any possible emergency use, being still in excellent operating condition.

We feel that the Sylvania 212-D tubes are most excellent and have recommended them to many of our technical friends in other stations, many of whom are now using them also.

We are more than pleased with the service these tubes have rendered at WFBE.

Very truly yours,  
R. W. F. Michael,  
Physics Department,  
Engineering Div.

tubes are definitely superior to other tubes.

Prove to yourself the economy resulting from the extra long service life of Sylvania Graphite Anode types, by specifying the purchase of Sylvania tubes in your next tube order!

The type 212-D has gone over big! The letter above tells the story. Can we say more?

© 1934, H. S. C.

## HYGRADE SYLVANIA CORPORATION


Hygrade Lamps

ELECTRONICS DEPARTMENT, CLIFTON, N. J.

Sylvania Tubes

FACTORIES: SALEM, MASS. EMPORIUM, PA. ST. MARYS, PA. CLIFTON, N. J.

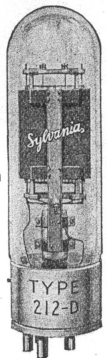WAREHOUSE STOCKS IN: Portland, Ore.; Atlanta, Ga.; Denver, Col.; Chicago, Ill.; Salem, Mass.; Dallas, Texas; Philadelphia, Pa.; Pittsburgh, Pa.; Los Angeles, Cal.




Sylvania  
Type  
212-D

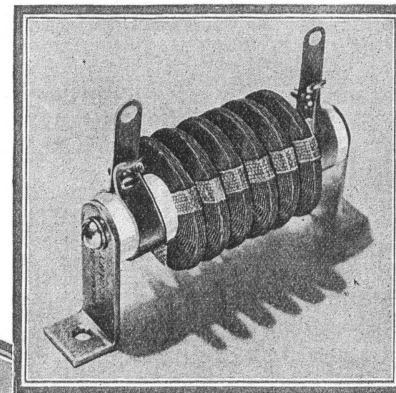
# HAMMARLUND

CHOKES are BETTER

BETTER in Design,  
Mechanical  
Construction,  
Electrical  
Features !



"CH-500" TRANSMITTER CHOKE

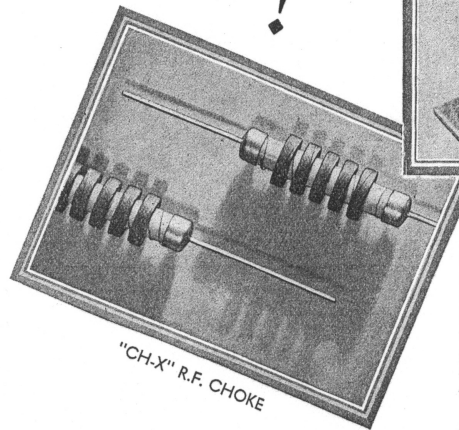

"CH-X" R.F. CHOKE

End caps are small, thin and so spaced that distributed capacity to adjacent coils is at a minimum. Inductance 2.1 mh. Isolantite core. Priced so low it can be used generously wherever R.F. filtering is desirable—such as detector plate circuits, all B+ leads, grid leads, etc. Only 75c each, less 40% to experimenters.

The Hammarlund "CH-500" Heavy-Duty Transmitter Choke delivers its highest useful impedance (more than 500,000 ohms) precisely where wanted—at the 20, 40, 80 and 160-meter amateur bands. Inductance 2.5 mh. Distributed capacity less than 1.5 mmf. DC resistance 8 ohms. Maximum recommended DC (continuous) 500 milliamperes. Isolantite core, with no metal through center. Mounts with a single machine screw, with brackets removed. \$1.75, less 40% to experimenters.

**D**ON'T be misled by similarity of appearance or claims. Know the FACTS! HAMMARLUND Chokes have been proved different and better in all essential qualities. As evidence, the Hammarlund "CH-X" is the smallest and lightest R.F. choke made. Its features are exclusive. Only 1/2" x 1 1/2", it is small enough for restricted spaces, and so light that the tinned copper leads are ample support. Leads extend straight from the end caps. This makes for neater wiring.

Mail Coupon for Details



HAMMARLUND MANUFACTURING CO.,  
424-438 W. 33rd St., New York

.....Check here and attach 10c for 16-page Hammarlund 1935 Short-Wave Manual, illustrating and describing most popular S-W circuits of past year, with schematic and picture diagrams and parts lists.

Check here for FREE information on Hammarlund Chokes.


Check here for FREE 1935 General Catalog.

Name.....

Address.....

PR-1

# Greater Power with GRAPHITE ANODES

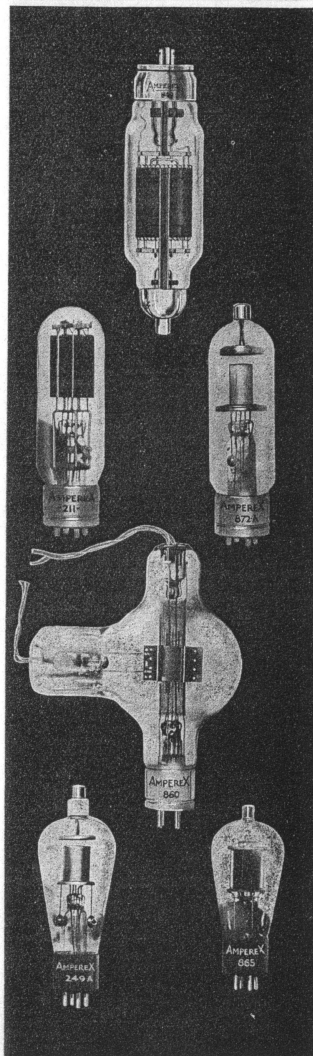

The cooler operation of Amperex Power Tubes—because of the greater surface and black body radiation of the Graphite Anodes results in longer life and greater power output.

## LIST PRICES OF AMPEREX TUBES

800 .....	\$10.00	*211H .....	\$ 17.50	852 .....	\$ 22.50
801 .....	5.00	212E .....	75.00	860 .....	35.00
203A .....	15.00	242A .....	12.50	864 .....	1.50
*203D .....	17.50	264B .....	1.75	865 .....	12.50
204A .....	95.00	276A .....	17.50	866 .....	4.00
205D .....	5.00	830 .....	8.75	866A .....	5.00
210 .....	2.50	841 .....	3.25	872 .....	15.00
211 .....	12.50	842 .....	3.25	872A .....	17.50
*211C .....	15.00	845 .....	17.50	869 .....	165.00
*211D .....	17.50	849 .....	160.00	869A .....	165.00

\*New High Frequency Tubes

Recent development work in the Amperex Laboratories has resulted in the perfection of several types of tubes particularly suitable for high frequency work in the Physio-Therapy and Diathermy fields, as well as for the amateur experimenter. These tubes, although in outward appearance and dimensions equivalent to 50 watt types, will in properly designed circuits deliver R.F. power outputs as high as 250 watts.

## AMPEREX ELECTRONIC PRODUCTS, INC.

79 Washington Street

Brooklyn, N. Y.

DISTRIBUTED BY

E. C. WENGER CO., Oakland, California  
 SAN FRANCISCO RADIO EXCHANGE, San Francisco, Calif.  
 RADIO TELEVISION SUPPLY CO., Los Angeles, California

# AMPEREX

Power Tubes •

BRANCH OFFICES:  
 New York City,  
 253 W. 128th St.  
 Tel. MOument 2-2812  
 Boston,  
 J. H. Condon,  
 6 Marlboro St.  
 Chicago,  
 C. W. Nelson,  
 3618 North Bernard St.  
 Los Angeles, Calif.  
 1455 Glenville Drive.  
 Tel. CRestview 4017

# RADIO

ESTABLISHED 1917 Reg. U.S. Pat. Off.

A NATIONAL MAGAZINE - PUBLISHED MONTHLY  
 Publication Offices—Pacific Building, San Francisco, California

Clayton F. Bane, Editor  
 D. B. McGown, Technical Editor.  
 Clair Foster, Amateur Activity Editor.  
 C. C. Anderson, Engineering Draftsman  
 H. W. Dickow, Business Manager.  
 Frank C. Jones, Ultra-Short-Wave-Engineering Editor.  
 George B. Hart, Contributing Editor.

25c per copy, \$3.00 per year by subscription in the U.S. \$4.00 elsewhere. Send subscriptions to the San Francisco office. Entered as second class matter at the Post Office at San Francisco, California, under the Act of March 3rd, 1879.

Vol 17

JANUARY, 1935

No. 1

## RADIOTORIAL COMMENT

### Worthwhile New "Q" Signals

WHEN an amateur CQs on the high-frequency end of the band it is generally assumed that he covers only that portion of the band when listening; he seldom goes beyond the middle of the dial. Thus those whose transmitters are tuned to the low-frequency end of the band are not often recognized by the high-frequency CQer, simply because he never gets to the other end of the band. Or vice versa.

A dyed-in-the-wool DX hunter covers his choice end of the band with great care, tunes slowly and depends upon his old acquaintances to answer his CQs. But the newcomer and the man who calls CQ for the purpose of raising anybody, anywhere in the band, has a different problem on his hands. Sometimes he starts to tune from the high-frequency end, sometimes from the other end. So that those who hear a CQ will know which end of the band the CQer will cover when he throws his switch to the receiving position, it is suggested by Art Bates of the CALL BOOK that a few new "Q" signals be added to the list. The suggestion is timely, should appeal to all good amateurs. Here are the proposed new signals:

QHM . . . I will begin listening at the high frequency end of this band, tuning towards the middle of the band.

QLM . . . I will begin listening at the low frequency end of this band, tuning towards the middle of the band.

QMH . . . I will begin listening at the middle of this band, tuning towards the high frequency end.

QML . . . I will begin listening at the middle of this band, tuning towards the low frequency end.

Although Mr. Bates has already sent these proposed new "Q" designations to various domestic and foreign radio magazines, it has been suggested by a staff member of "RADIO" that the new signals be reduced to two in number, i.e., one signal to indicate that the operator is tuning from the high frequency end of the band towards the middle, and another signal indicating that he will tune from the low frequency end of the band towards the middle. QLO would indicate, "I start tuning from the low frequency end." QHY would indicate, "I start tuning from the high frequency end."

Thus only two new signals would be added, both self-evident in character, the "LO" portion of the "Q" signal automatically means "LO Frequency" and "HY" means "HIGH Frequency." "I would be better to make it QHI instead of QHY, but for the laugh that HI has associated itself with.

An expression from the reader is asked for. Quick action is needed so that the new signals will be widely known and used when the next international tests are with us. Do you favor four new "Q" signals as suggested by Bates, or only two new signals—QLO and QHY—as suggested by "RADIO"?



### Thank You, Ever So Much!

THE destiny of amateur radio is in the hands of Congress," you were told by the Political Editor in December "RADIO." And a flood of letters from subscribers—far too many to answer individually, are stacked high in the editor's files. How to approach a Congressman? That's easy. Colonel Foster will present the plan in full in the next issue of this magazine. If you are seriously interested in the future welfare of amateur radio, you will

our Government or to our people, so that we will still be AMATEURS when the time of need arrives. If you thrive on fact, not fancy, you will find a lot of it in next month's "RADIO." Colonel Foster knows Washington and Washington knows Foster. Thus the constructive program of telling the amateur what to do and how to do it will be presented with full vigor in the months to come.



### The First Successful 5-Meter Super

ELSEWHERE in these pages you read what Frank C. Jones has accomplished in the form of 5-meter reception via the super-heterodyne tube. Again, necessity was the mother of invention. The 5-meter band is already overcrowded in many of the larger metropolitan areas. The super-regenerative receiver must soon give way to inexpensive forms of 5-meter super-hets. Until this time there has not been available a WORKABLE super for the ultra-high frequencies. The latest achievement of Frank C. Jones will be welcomed by experimenters, manufacturers, jobbers and retailers.

May this latest contribution to the art bring you greater pleasure and more thrills from your 5-meter experiments.

TALKING about Frank C. Jones, turn back the pages of "RADIO" to 1925. Nine years ago, Jones was at work in his laboratory, conducting a series of transmitter amplifier tests. The amplifier was coupled to the antenna by means of two wires. Accidentally, Frank Jones moved the feed wires closer together, found that the output was increased. Thereupon he twisted the two wires together and observed a marked increase in antenna current. And so "Link Coupling" was discovered. Unquestionably, this form of coupling has played one of the major roles in modern amateur practice; it seemed reasonable to assume that Link Coupling could also be applied to receiving equipment. Consequently, Frank Jones went to work to find out what would happen when an antenna is link-coupled to a detector circuit. Also in these pages is an article from his pen, telling how to build a marvelous little amateur superheterodyne receiver which uses this new form of antenna coupling. If you like to "roll your own," here is your opportunity to build a receiver that is literally a hair-raiser. Thus "RADIO" starts the new year right, with a pair of editorial scoops that should be welcomed by all. The technical standard of the magazine will be vastly improved during 1935. It will be an exciting year for the radio amateur.




Uncle Sam to Amateur Radio Spokesman:  
 "If it's more privileges you want, why not come up and see ME sometime?"

heed his timely advice and join the vast army of amateurs who have already pledged themselves to leave no stone unturned to prevent the frequency-grabbers from ultimately putting V-wheels on sacred amateur territory.

Fortunately for the amateur, the President of the United States is a man of vision. Every amateur is ready to back him in the event of national emergency. We are going to ask him to back us, without a penny of cost to

# A Deaf Mute Asks for an Amateur License

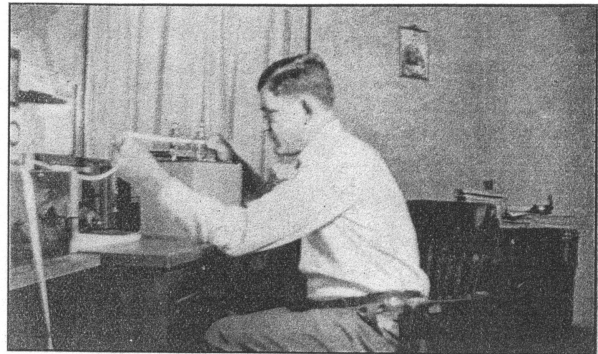**\* If this story does not make your heart throb, you are not worthy of the name "amateur". For here is an appeal to every radio amateur in the United States to do his small part in helping Mr. Adolph Czajka of Chicago in his efforts to secure an amateur license. Petitions from radio clubs should be sent directly to the Federal Communications Commission at Washington.—Editor.**



Adolph J. Czajka at the tape recorder. He will send you a piece of the tape on request.

**T**O**TALLY** deaf, he hears all over the world. Mute, he understands the language of the far places. In thirty-six countries of the globe his name is known but his voice has never been heard. And now 15,000 persons are asking Washington to abrogate federal regulations in order that he may have a tongue. Introducing: Adolph J. Czajka, deaf mute radio operator of 2428 West 34th Place, Chicago, Ill.

Adolph is one of the world's most remarkable people. Totally unable to hear a sound he is a first-class radio operator. In his humble home where he sits through the long nights, and silent days, he has 900 QSL cards from "hams" from all over the world. He has never heard a signal from any of their stations. In place of ears that will not function, Adolph uses his eyes—that and a recorder of his own design.

Adolph "sees" radio signals. Incoming continental is logged on a tape and becomes to this man who lives in a world of silence, living speech from the outside world. Thirty—forty words a minute his little chattering recorder plods away and through it Adolph Czajka knows the gossip of the air-planes. He saves his tape and sends it to fellow hams so they may see a picture of their sending—good or bad. And they thank him for it.

It is the great dream of Adolph's life to own a federal amateur license. Regulations provide that he must copy audible signals in order to be licensed as an operator. But a movement has been started by fellow operators to have federal regulations waived in his behalf. The need is imperative. Through radio a new world has been opened to this man who cannot hear and who must depend upon the lightning speed of his fingers for communication with others.

"I cannot be without my radio", he writes on his typewriter, with a world of pent-up feeling behind the words. "I like very much to be radio ham or fan better than to go

around bums on the street. My wife says if I stay at home with my short wave receiving station I will be a good man."

And so Adolph stays home and listens to his fingers. He wants to talk back. He knows the code. He can handle a key. He knows how to build his transmitter. All he needs now is for Uncle Sam to temper

birthrights, Adolph years ago turned to radio and found there an electrical voice he could see with his eyes. Thereafter a new world was opened to him.


One of Adolph's friends—operator on the U.S.S. Pontchartrain at Norfolk, Va., wrote to him, expressing a hope that the federal body would grant him a license. "We all think here it would be a dirty shame not to," he wrote. "You could have my ticket if there was any way of giving it to you. I know it would mean a lot."

Only Adolph Czajka knows what it would mean to break the radio silence of 12 years—to reach out, touch a key with hungry fingers and through the tiny spots on his recorder tape learn for the first time that his far-flung radio impulses had been received. To talk, in other words, for the first time in his life, through the necromancy of the new science that has linked the countries of the world in a new understanding.

That is the New Year's gift that radio hams of the United States are seeking for this undaunted hero of the air lanes through petition to official sources. How they feel about it is shown by some of the scores of letters in which fans express their thanks to Adolph for the real service he has done ham radio by his soundless check on transmitted signals. One from W8IZE at Clarke Summit, Pa., in point:

"Thank you very much for your tape recording of my signal . . . while examining the tap I notice I have a tendency to hold the last dash in '8' w' and 'z'. I am glad to know this and will try to correct that to improve my keying. Sure hope you are successful in obtaining a special license to operate. You ought to work it up with a tape recorder. . . 73."

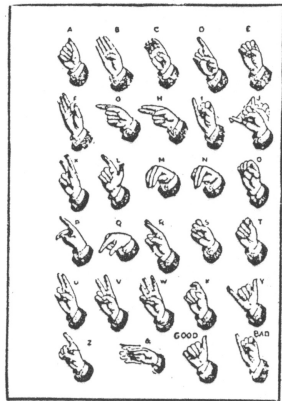From 9WL at Chicago came this one: ". . . fb on your building your own recorder. Your good work speaks for us."



This—and the radio code—are the only languages that Adolph Czajka knows. The illustration above depicts the "sign language" of the deaf mute. It is reproduced from his QSL card.

great interest that radio can stir up in people, surely handicapped as you are. I think it is marvelous. I hope you have good luck."

From W8BCV at Detroit: ". . . I am writing a letter to the ARRL (Continued on page 18)

# I Voted "NO"

By COL. C. FOSTER, W6HMM

**A**T THE Fresno convention a motion was made to split the Pacific Division in two and make the southern half a new division. It was made by W. W. Matney, W6EQM, the ranking officer of the new little group with the new big name, "Federation of Radio Clubs of the South-west, ARRL, a California Corporation". Generally speaking, resolving at ham gatherings is merely a form of pastime and about as futile as praying for rain in Death Valley. The accompanying arguments do, however, give us a chance to blow off steam. Some of us like to "debate", some of us blow tin whistles, some hammer out calls on the steam pipes.

Some of us ease the pressure merely by "seconding" motions and casting votes in all directions—long, loud and often. As most pressures are largely in their anticipation, we hams get ours from the pictures our wishes present in these "resolutions." The fact that their objects are seldom realized and always soon forgot takes none of the pleasure from the making of them.

We older hams who are more or less "sales-proof"—more or less immune to herd emotionalism—vote perfunctorily if we vote at all. We know perfectly well that when a ham assemblage votes to raise the power limit of stations it has just as much effect on the Federal Communications Commission as throwing stones at the moon. There is an intelligent and forthright way of getting more power for amateur stations but men of experience know that firing broadsides at ONE ANOTHER at hamfests will never get it.

But occasionally there appears a resolution that concerns only the machinery of the amateurs' own organization. Such movements do hold the possibility of bearing fruit—sweet or sour, as the case may be. This motion of the "Federation" to secede from the Pacific Division and force Southern California to become a part of a new division was of this nature—an internal ARRL affair. The younger element of the south had been well proselytized in advance, so there were many pairs of lungs under high compression with suppressed "Ayes". When the chairman called for these eyes the hall was filled with them. Surmising that there would be few "Noes" I put plenty of steam back of mine to make it go as far as possible. And I had the proud distinction of voicing the ONLY "no". Perhaps "Ten thousand Frenchmen can't be wrong", but I'll swear that one hundred hams can—when well narcotized beforehand. I was asked if I would be willing to give my reasons for voting "no." I replied that I would do so in writing. I hereby do.

This plan of the Little ARRL, Incorporated, however sinister, is fairly easy of accomplishment, provided the Warner-Segal-Maxim combine desires it. That combine, the key man of which is Warner, controls a majority of the ARRL directors. It controls likewise the executive committee, all of the acts of which are invariably accepted by the ruling majority of the board as their own acts.

Warner encountered no obstacles in throwing the Philippines out of the Pacific Division and actually disfranchising the Philippine members in 1930. This was done not only without the knowledge and consent of the Pacific Division but even without the knowledge of the Philippine members themselves! And the Philippines STAYED out until 1932—until Warner was apprised by the then director of this division that unless the Philippine members were restored to their rightful status he and the directors would be taken into court and FORCED to put them back. Now, if Warner could engineer such a violation of all the canons of courtesy and justice as that he could as easily, with the backing of this resolution of the Little ARRL, Incorporated, remove Southern California and Utah, (or any other state), from the Pacific Division. In the Philippine case Warner made the mistake of keeping the project secret from the division members. I suspect that in the present case he is avoiding his former mistake by permitting the present plan to "originate" in an open meeting of Pacific Division amateurs—even though only 155 of the 536 registrants at this convention claimed membership in the ARRL. In which event he would have an alibi such as he failed to provide for himself in the Philippine case. History has a way of repeating itself and the amateur who is unacquainted with it or ignores its lessons is losing the greatest opportunity for seeing what is going on under the surface today.

The Little ARRL, Incorporated, is a federation only in name. The association of the amateur body with it is loose in the extreme. Its members are such of the southern clubs as have joined it. Its meetings consist of its officers and such "delegates" of the member clubs as put in an appearance. The rank and file of the clubs know little and care less of the inner workings of Little ARRL, Inc. The scheme is to make a small group appear to be speaking for a large body of amateurs—to make the Little ARRL, Inc., appear to be speaking for all the amateurs of Southern California, just as the Big ARRL, Inc., has conveyed the impression that it is composed wholly of amateurs and that it speaks for all the amateurs of the United States, while in fact it is composed largely of commercial radio people and other non-amateurs with only a small proportion of the amateurs of America in it. Its motivation is essentially the aim of a few men to dominate the amateurs of Southern California, regardless of how few may have any interest in either the Little ARRL, Inc., or the Big ARRL, Inc. However wholehearted may be the moving spirits of the Little ARRL, back of it all lies the aspiration to shine as IT.

It is common belief that this group of secessionists is a Warner outfit. There is much evidence to substantiate the belief. The character of correspondence between the group and the ARRL headquarters points to it. And last year when the San Jose Club—long vilified by headquarters—sponsored the division convention, no headquarters man was sent to it—while not long afterwards when the newly hatched "federation" worked up a hamfest under its own name Warner sent his right-hand man, Budlong. The only instance of which I have heard of the ARRL's money being spent to send a man clear across the continent to a mere hamfest. At the Fresno convention it was again Budlong. Much of his time was spent in the company of officers of the Little ARRL. And after the convention he was again with them in and around Los Angeles. If Budlong had disapproved of the Federation's plan to disrupt the Pacific Division it is a cinch that Matney would never have offered his resolution. The plan must have had the approval of Budlong's tacit approval. It would not have had his approval without having Warner's approval. So much is certain; for with Budlong as with everyone else on Warner's staff he plays Warner's game or he loses his job.

And fat jobs aren't picked out of the bushes these days.

Officers of the Little ARRL definitely approved Warner's action in failing to report the truth of the Madrid convention. They approved of Warner's actions in Washington against the efforts of amateurs all over the country who were striving to prevent ratification of the new amateur restriction, thus providing the spectacle of a group of amateurs siding with the commercial element that had contrived the new restriction—the spectacle of Pacific Division amateurs approving a new restriction devised for killing the greatest continuous public service ever performed by the amateurs (and performed almost wholly by Pacific Division amateurs)—the trans-Pacific traffic. So when we call this group of secessionists a Warner outfit we do so with deep conviction.

The proponents of the secession plan had only two reasons to advance for it. They had some arguments besides, but when their talk was divested of inconsequential and irrelevant reasons boiled down to just two—(1), That Mr. Culver, director for the division, lives too far from them to come and see them as often as they would like, and, (2), That the ARRL members of the division are so numerous they cannot be properly represented by one director at the yearly meetings of the board.

As for No. 1—There are some wise, grown-up amateurs in Southern California, and in all the years of the Pacific Division's existence none of these men has ever intimated that a director residing in the San Francisco area was too far away. Anyone in any part of the division who wishes to confer personally with the director is welcome to do so. If a man wishes to see the director there is no reason why the director should always be the man to do the traveling. The director attends a number of important gatherings each year in different parts of the division. There is no reason why a director should attend every hamfest, nor does he—even in his own vicinity. If he had no better use for his time than running to hamfests all over the map he would not be exhibiting the common sense needed for a director. Perennial playboys and glad-handers don't make dependable directors. In all the history of the division no intelligent ham ever before kicked because the director resided approximately in the middle of the division. And just remember that Hawaii and the Philippines are also in the Pacific Division.

Claim No. 2 is wholly specious. The truth of the situation is that the secessionists don't like Culver. If they did, it would not have occurred to them that they themselves needed a different director. In their dislike for Culver they are disclosing either that they cannot recognize outstanding ability and character or else that they are taking their cue from someone else who doesn't like him. The ARRL headquarters does not like him; and for the sufficient reason that of all the directors at present on the board he and Director Jobs are the only two who are bent upon cleaning up the mess the ARRL is in. This is the common knowledge of discerning amateurs throughout the United States.

Just presume, for the sake of argument, that the secessionists had got their new division. They would, of course, expect to name a man of their own way of thinking as its director. Now, at the last meeting of the ARRL board, 14 of the 16 directors approved Warner's Madrid conduct just as did the secessionists; so the men of the Little ARRL, Inc., cannot well maintain that they need

(Continued on page 38)

# The First Practical 5-Meter Super

By FRANK C. JONES  
Ultra-Short Wave Editor

The writer, in common with other 5-meter experimenters, has always had better luck with super-regenerative receivers than with any other type on the 5-meter band. An analysis of the situation brought out some interesting points, so another superheterodyne receiver was built and the results have been very gratifying. The sensitivity and selectivity of this receiver is better than any super-regenerative receiver that I have ever tested.


For present day purposes, a receiver must tune broadly enough to cover from 50

The RF stage provides a little additional gain where it is really needed, reduces image interference, and removes antenna resonance absorption spots from the regenerative circuit. This combination brings in 5-meter signals that are inaudible on super-regenerative sets using a stage of TRF. The same results were obtained in comparing it with an ordinary transceiver set.

vide maximum sensitivity, delayed AVC was used and this voltage applied to the grids of the two IF stages only. An audio volume control is used to maintain the desired amount of loudspeaker volume. The sensitivity control, a 50,000 ohm IF cathode variable resistor, could have been made 5,000 or 10,000 ohms with a slotted shaft for screwdriver adjustment only, since the usual field strength of 5-meter transmitters is quite low.

Examination of the circuit will show that the RF and detector circuits are quite similar to those used in longer wave sets. These two circuits are tuned by a gang condenser made from a couple of midget condensers. The condensers were originally 100 mmfd and later were double spaced and only 7 plates left in each condenser. Double spacing helps on 5 meters since the condensers are less microphonic when the loudspeaker is being operated at good room volume. Trimming the detector and RF stage is accomplished by means of the semi-variable coupling condensers from the antenna to grid, and plate to grid of the respective stages. The coils were made of No. 14 wire so the inductances can be varied by slightly altering the turn spacing. No attempt was made to track the oscillator with the other two circuits, although this could probably be accomplished. Regeneration makes the detector tuning about as sharp as that of the oscillator.

The second detector and audio power stage is quite similar to that used in some broadcast receivers. Delayed AVC is obtained by using one of the diode plates biased with respect to the cathode. The signal must be of a certain amplitude before any negative AVC voltage is generated for AVC control. The audio frequency is taken from the other diode plate without any bias, since the latter would cause audio distortion. The high mu triode section of the 75 tube is used as a regular resistance coupled audio stage giving a gain of about 40 to 50. A type 42 pentode increases the signal to loudspeaker volume. A tone control is provided to reduce automobile ignition interference which is quite serious when using a superheterodyne receiver in most locations. A high half-wave receiving antenna, transposed two wire feeders and an electrostatic shield should reduce

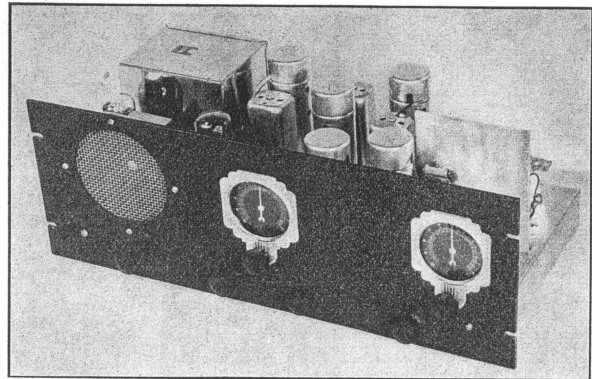


The front panel presents a symmetrical and pleasing arrangement. The loud-speaker is protected with a metal grille. Illuminated Crowe airplane tuning dials add beauty to the job. The panel is of standard relay rack.

to 100 KC band width in order to receive the usual modulated oscillator transmitter signals. Very few stations use crystal or MOPA controlled sets and thus a special IF amplifier was built using a short wave about 110 meters for the intermediate frequency. This, with close coil coupling, gave a nice band width and the superheterodyne therefore becomes really practical for present day service.

A superheterodyne receiver for police 8-meter work should also tune broadly, since even with MOPA or crystal control in the car sets, the main station must have a stand-by service without constant retuning. The ordinary first oscillator in the superheterodyne will drift from 20 to 80 KC as its temperature changes and with variations of line voltage. This means that the IF amplifier should be broad enough in its tuning to take care of this oscillator drift. The car transmitters are also liable to drift; therefore the IF amplifier should be broad.

Most 5-meter superhets have lots of noise and very little signal. The trouble usually lies in too much IF gain and not enough RF gain ahead of the mixer tube. A straight RF amplifier will provide some gain, but regeneration is the real answer. Regeneration at the IF frequency does no good, but it can be used in either the RF stage or in the detector grid circuits. Both methods were tried and best results were obtained by using regeneration in the detector circuit, since antenna resonance has no effect of dead spots in the regeneration control. Better weak signal response from a signal generator was obtained by using first detector cathode pad regeneration than when the same method was used for the RF tube.

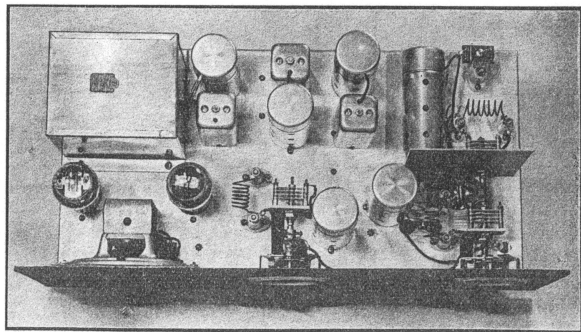

Looking down into the 5-meter Super. The RF coil is mounted horizontally to permit the use of very short leads. An aluminum shield isolates the RF stage from the detector. The inductances are mounted on porcelain stand-off insulators. The power transformer is at the left end of the chassis. It is the new UTC Nikshield unit, with 6.3 volt filament winding. The midgrid dynamic speaker is a 5-inch Magnavox.

this trouble. The antenna coupling condenser should then be connected across the tuning condenser and a Faraday electrostatic shield placed between the tuned grid coil and tuned antenna feeder coil. Most of the auto QRM is picked up in the down leads and is transferred beautifully by even the slightest bit of capacity coupling. The receiver should be mounted in a relay rack with a metal dust cover, or in a metal cabinet if used on a table or desk. Too much emphasis cannot be placed on the need of using an efficient, noise-reducing type of receiving antenna.

Several oscillator circuits were tried and best results were had from a 76 tube instead of the usual electron coupled 6C6 or screen grid tubes. A form of electron coupling is used to the mixer tube because the suppressor grid is used for that purpose. This puts the suppressor grid at a positive potential of about 100 or so, since it ties directly to the oscillator plate. However, this seems to give better conversion gain in a regenerative detector than any other system tried. Invariably, comparisons between capacity coupling or any other form and this method, gave the latter the edge by about two or three times in sensitivity.

The receiver is mounted on a 7 x 19 x 7/8-inch aluminum panel for relay rack mounting. The holes for the loudspeaker opening and the two airplane type dials can be cut by means of a flying bar cutter. The chassis was made of No. 14 gauge aluminum because it is easily drilled and does not require plating. The chassis measures 9 x 17 1/2 x 1 1/8 inches. The pictures of the set give a good idea of the general layout of the parts. The signal comes in at the grid of the horizontally-mounted RF tube, through the first detector, two IF stages, second detector and power audio stage. The power equipment and loudspeaker are mounted at one end and the RF portion at the other. The IF amplifier occupies the rear middle portion and the high frequency oscillator the front middle portion. The oscillator tuning condenser must have an insulating coupling to the dial because this circuit is "hot" at both ends of the LC circuit.

The two radio frequency chokes were made by winding about an inch of winding length of No. 34 DSC on a 3/8-inch diameter bakelite rod. All of the coils were made of No. 14 wire, space wound on a half-inch diameter. These coils are mounted on small stand-off insulators near the tuning condenser terminals and they can be changed


in a few minutes, if the receiver is to be used on some other short wave band.

The RF tube was mounted horizontally so as to obtain a short plate lead to the detector grid circuit. All of the RF stage by-pass leads are very short and return to the common ground point on the RF partition shield. By making this point at the tuning condenser rotor connection, interlock between the RF and detector circuits is avoided. Short leads are necessary in 5-meter work because an extra inch of wire adds quite an appreciable value of inductance.

The IF amplifier uses about 2.7 MC as its frequency. The transformers were home-made affairs, using the parts of regular IF

and were made by pulling off 40 feet of wire from each coil and closing up the coupling until adjacent coils were 3/4-inch apart. The IF frequency was adjusted to 1550 KC, but the selectivity was a little too great and the image interference was troublesome. The higher frequency of 2700 KC or 2.7 MC proved to be best. So far no trouble has developed due to IF amplifier pick-up from the antenna circuit on 110 meters. This is minimized by the use of the RF preselector stages and shielding.

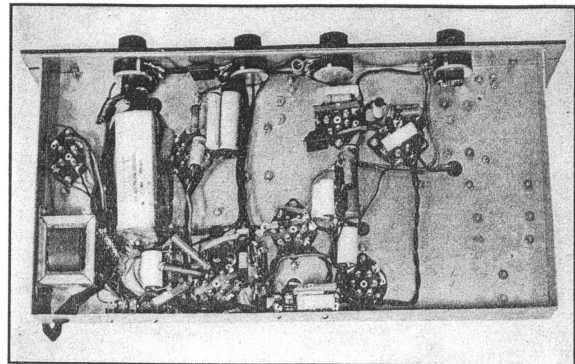The IF amplifier should be lined-up by means of a modulated oscillator of the all-wave type. Starting from the second detector circuit, each stage should be aligned by




Under-chassis view, showing proper location for filter choke and condensers.

transformers. Those used in this set were wound on 3/8-inch diameter tubes. The 450 KC litz coils were removed and two windings each of 120 turns of No. 34 DSC wire put on in jumble fashion to cover a winding length of 3/8-inch. 3/8-inch spacing was used between adjacent coil edges. These windings, tuned with the mica trimmers of the original transformer, cover from approximately 100 to 120 meters. If one lives very close to a 120 meter police station it would be desirable to use about 100 turns and tune the transformers to about 90 or 100 meters. The first transformers tested used litz wire

coupling to the oscillator, then a recheck made of the overall amplifier by coupling the oscillator into the first detector grid circuit. The latter should connect temporarily through a 1000 ohm resistor to ground instead of to its LC circuit, while aligning this IF amplifier.

Alignment of the RF and detector stages is fairly simple. The detector coupling condenser should be adjusted until its capacity is low enough to allow the first detector to break into oscillation when the regeneration control is on full at both ends of the tuning range. The RF antenna coupling, or trimmer condenser, should be adjusted together with slight coil turn respacing until the noise level is highest throughout the band. There is usually enough noise from auto ignition to accomplish this, although a harmonic signal from a modulated all-wave oscillator is much superior for this purpose.

An interesting test was made with a signal generator and a small radiating antenna. A regular receiving antenna was first connected to a good super-regenerative receiver and the signal attenuated in the generator until it was just barely noticeable in the high background noise of this form of receiver. The super-regenerative was then replaced with the superheterodyne receiver and this same signal gave loudspeaker volume without the background noise of the other set. The absence of background hiss is especially pleasant when comparing the two sets for loudspeaker operation. When the auto ignition noise level is low, the 5-meter signals roll in and out without any fuss or change of hiss level, making it difficult to tell an R9 signal from an R6 signal. If the local flashing sign or auto ignition QRM is high, the 5-meter signal strength can be judged by the amount that it overrides the noise level.

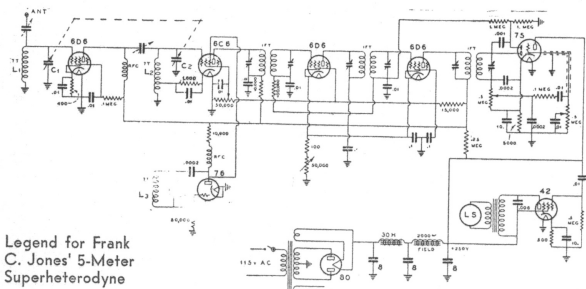

Legend for Frank C. Jones' 5-Meter Superheterodyne

L1 and L2—Each 1 1/2 in. long, 7 turns, No. 14 enameled wire, 1/2-in. dia. turns. L3—1 in. long, 7 turns, No. 14 enameled wire, 1/2-in. dia.  
C1, C2, C3—100uufd. double-spaced variable condensers, with only 7 of the original plates remaining. Maximum capacity of these re-built condensers to be about 18uufd.  
I.F. Transformers tuned to approximately 2,000 KC.





# The "222 Communications Receiver"

An Efficient, Simple and Inexpensive Superheterodyne

The Antenna Is Link-Coupled To The Detector

The Receiver Employs Regeneration, Tone and Volume Control, One Stage of I. F. and Other Useful Features

By FRANK C. JONES

• This receiver was designed for the amateur who likes to build his own sets and who is primarily interested in three band operation. The parts are available from most radio supply houses and the cost is not excessive. It is the next logical step from a TRF receiver and costs much less than an elaborate crystal filter superheterodyne. The set will cover the 20 and 40 meter amateur bands without coil changing, which is a convenience when one is interested in two bands, such as 20 and 40 meters. For 80 meter operation a separate set of coils is needed.


The receiver is very sensitive on 20 and 40 meters due to the special first detector

pressor grid works fine in giving a very sensitive regenerative first detector.


The first and second oscillators are orthodox electron-coupled circuits with good frequency stability. The first oscillator is made to oscillate strongly for good conversion gain, while the second one oscillates weakly to minimize harmonics which would cause steady beat note whistles in certain spots in the short wave range. Adjustment of this oscillator strength and twisted

and audio amplifiers. The audio amplifier uses the headset as a bias resistor for this tube, with the tone control across the phones. This connection allows the telephone jack to be grounded to the aluminum chassis or panel. The grid circuit audio signal is confined to the grid and cathode by means of a 0.1 megohm resistor and a 0.1 mfd by-pass from the audio transformer to cathode. This prevents any audio degeneration and loss of signal—so the output is the same as if a cathode resistor and large by-pass condenser were used and the headset placed in the usual place circuit.

A separate power pack is used. B bat-

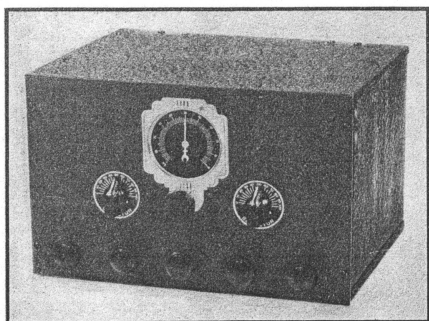

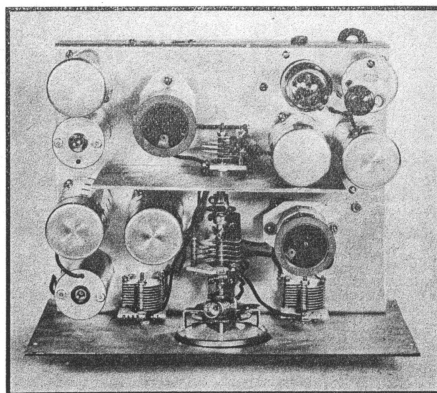• One set of coils covers both the 20 and 40 meter bands. A separate set of coils is used for 80 meters. The illustrations show the front view and the interior arrangement of parts. The receiver is A.C. operated, but it can also be used with batteries if 6.3 volt tubes are used.



circuit employed. Regeneration is used and a variable antenna coupling allows maximum effect from the regeneration. The antenna coupling is a simple unit using a sliding rod, knob controlled, and a sliding coil. Link coupling is used between the antenna coil and the first detector coil and one of these link coils is slid back and forth for variable coupling. This also minimizes capacity coupling to the antenna without using a Faraday electrostatic screen, thus reducing man-made static. The same antenna and link coil assembly are used on all bands, thanks to the link coupling as applied to receivers.

Regeneration is obtained by means of a cathode tap on the detector coil because this gives a more uniform regeneration effect over the wide range of any one set of coils. The conversion gain of this detector is very high, due to regeneration, and to the method of oscillator coupling used. The suppressor grid connects directly to the plate of the electron-coupled oscillator. This practically eliminates oscillator radiation into the antenna because the screen grid is by-passed to ground and electrostatically shields the suppressor grid from the control grid circuit. The positive potential on the sup-

wire coupling capacity to the second detector grid also allows maximum signal to BFO noise ratio. The use of a high plate and screen grid resistor limits the harmonic output and simplifies the shielding problem for the BFO. A strong oscillator for the BFO means that it should be double-shielded and usually results in high noise level in the audio output. This trouble has been eliminated in this receiver.

The IF amplifier uses only one stage because two stages complicate the set and provide more noise than signal, unless a crystal filter is to be used. With only one high gain IF stage operating at about 500 KC, no isolating condensers and resistors are needed in plate, screen-grid and cathode circuits. An IF and audio volume control are both provided because often low audio gain and high IF gain will pull a weak signal into readability through the noise level.


A stage of audio amplification is used to provide a method for audio and tone control and also more gain when necessary. The set is designed for headset operation but has actually enough volume to drive a magnetic speaker to good volume on signals that are well down into the noise level. The type 76 or 56 tubes make good power detectors

and a 6-volt storage battery can be used, providing the on-off switch external to the set cuts both A and B leads in the off position.


The IF amplifier uses a pair of the new iron-core transformers which have a little better selectivity and gain than the ordinary air core type. They are tuned by means of trimmers, like any other IF transformer. If these transformers are not available the usual air core units can be used with entire satisfaction.

In any of these IF units, the coupling has been adjusted at the factory for best broadcast reception gain and band width. This is generally too close for best short-wave practice where greatest selectivity and good gain are desirable. The two coils should be at least an inch apart and 1/4 inches works very well with most small air-core IF transformers. Some makes can be adjusted by warming the supporting tube with a soldering iron tip until the wax softens, then sliding the coils apart. The iron core transformers have a pair of coils mounted at right angles to each other on short molded straight cores. Coupling is adjusted by a screw adjustment on the lower coil which slowly moves it along its axis.

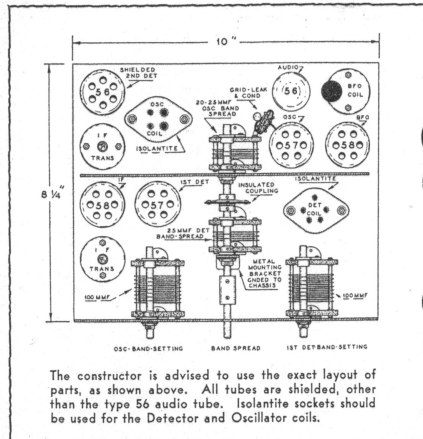As previously stated, a single stage of IF



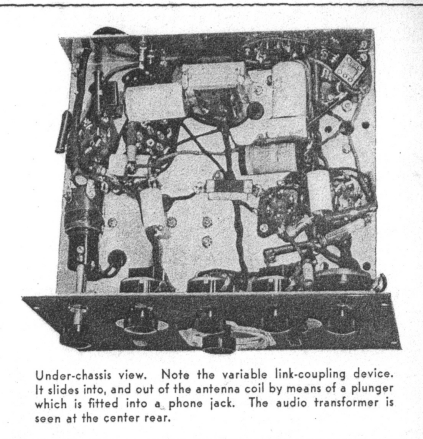The constructor is advised to use the exact layout of parts, as shown above. All tubes are shielded, other than the type 56 audio tube. Isolantite sockets should be used for the Detector and Oscillator coils.



Under-chassis view. Note the variable link-coupling device. It slides into, and out of the antenna coil by means of a plunger which is fitted into a phone jack. The audio transformer is seen at the center rear.


will give ample gain if the front-end of a super is functioning as it should. A stage of RF ahead of the first detector is sometimes desirable, but it does not compare with a super using a regenerative first detector unless regeneration is used in the RF stage. This adds complications and means another ganged circuit, which does not simplify the set. The present set uses a ganged oscillator and detector circuit because both of these circuits have 100 mmfd padder or band-setting condensers controlled from the front panel.

The oscillator tuning condenser is a double spaced midget condenser of eight plates while the detector condenser has nine plates double spaced. These condensers were made from 100 mmfd Cardwell "Trim-Air" normally spaced midget condensers, similar to those used for band setting. By winding the oscillator to cover a greater winding space of 1 1/4 inches as against 1 1/8 inches for the detector coil, the oscillator and detector will track throughout the narrow amateur bands. With the number of plates left in these double spaced condensers, the 20-meter band covers about 15 divisions on the airplane type dial and the 40-meter band about 60. Greater spread can be had by removing plate from each of these condensers. A flexible coupling should be used to gang the oscillator condenser to the front detector condenser so as to eliminate torsion detuning effects on the beat note of a CW station, which always occurs with any dial and condenser mounting.

The antenna system uses a shielded lead-in pair which connects directly to the fixed antenna coil underneath the chassis. This eliminates binding posts and unwanted pickup and presents no complications since the shielded pair can be insulated with tape from the underside of the chassis terminals. The antenna coil consists of 12 close wound turns of No. 24 DSC on a 1 1/4 inch diameter bakelite tube about 1 1/4 inches long. The sliding coil is of 4 turns close wound of No. 24 DSC on a 1-inch diameter tube. Flexible leads form the remainder of the link coupling device to the isolantite coil socket above the chassis. Four turns of this same wire were wound on the detector coil about 1/2 inch from the ground end and thus very little capacity coupling exists between the antenna and first detector coil. This 1-inch bakelite tube is controlled from the front panel by means of a plunger action

knob over a distance of about an inch. This knob has a 3/4-inch diameter brass rod extending through the front panel and fastened to the 1-inch tubing with a couple of machine screws. The bearing and retaining or pressure spring is simplicity itself, being an ordinary short telephone jack. The rear tip connection acts as a pressure spring against the brass rod and it remains in whatever position it is adjusted to with the knob.

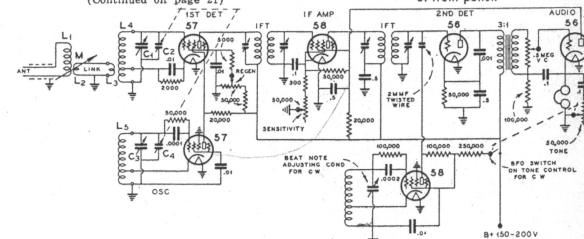This antenna coupling device is well worth (Continued on page 21)



FRANK C. JONES' 222 COMMUNICATIONS RECEIVER

Coils L1, L2 and L3 are the same for 20, 40 and 80 meter operation. L1—12 turns, No. 24 DSC wire, close wound, on 1 1/4 in. dia. tubing.  
L2—4 turns, No. 24 DSC wire, close wound, on 1-in. dia. tubing. This coil slides into coil L1; the coupling is made variable by sliding L2 into and out of L1.  
L3—4 turns, No. 24 DSC wire, wound on 1/2-in. dia. tubing, separated 3/4 in. from L4.  
For 20 and 40 meters: (same coils used for both bands).  
L4—11 turns, No. 18 DCC wire, space-wound on 1 1/2-in. dia. tubing, to cover a winding space of 2 3/4 in. long, and tapped at one and one-third turns from bottom.  
L5—11 turns, No. 18 DCC wire, space wound on 1 1/2-in. dia. tubing, to cover a winding space of 2 3/4 inches, and tapped at 2 1/2 turns from bottom.  
C1-C3—100ufd. midget variable condenser.  
C2—9 plate double-spaced midget condenser to give approx. 250ufd.  
C4—7 plate double-spaced midget condenser to give approx. 250ufd.

(Use 8 plates for C2 and 6 plates for C4 if more band-spread is desired).  
Condensers C2 and C4 are standard Cardwell 100ufd. "Trim-Air" midgets, with alternate plates removed so as to double-space the plates.  
L1, L2, L3 same as for 20 and 40 meter operation.  
L4—30 turns, No. 24 DSC wire, wound to cover a space of 1 1/2 in. on a 1 1/2-in. dia. form, with cathode tap taken at one turn from bottom.  
L5—26 turns, No. 24 DSC wire, wound to cover a space of 1 3/4 in. on a 1 1/2-in. dia. form, with cathode tap taken at 4 3/4 turns from bottom.

NOTE—The cathode tap on the oscillator coil must not be too high, otherwise image interference will become serious.

TUBES—Instead of using type 56, 57 and 58 tubes, this receiver will give equal satisfaction if the types 606, 606B and 76 are used for 6.3 volt operation.  
160 METER BAND—This receiver will not operate successfully on the 160-meter band unless large variable condensers are used in place of the small midgets. The receiver was primarily designed for 20, 40 and 80-meter operation.


Band	CONDENSER SETTINGS		
	Oscillator Band-Setting Condenser	Detector Band-Setting Condenser	Coverage on Main Tuning Dial
20 Meters	8°	10°	12° to 15°
40 Meters	80°	95°	50° to 60°
75 Meter Phone Band	45°	50°	25°
80 Meter C.W. Band	50°	55°	100°





# New 5-Meter Developments

## Jacobs' Duplex Transmitter-Receiver

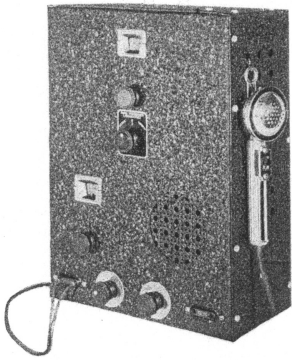

Exterior View of Radio Transceiver Laboratories Duplex Transmitter Receiver

THE Radio Transceiver Laboratories Type 53-6A6 Duplex Unit employs a radio-telephone transmitter similar to that of the Jacobs' 53-6A6 Transceiver. Like the transceiver, it employs twin-triodes, unity coupling and class B modulation; but in addition, the TR unit has a separate four-tube super-regenerative receiver and a dynamic speaker. Receiver radiation interference is eliminated and duplex operation is thus made possible. Duplex, or break-in operation is two-way transmission and reception, similar to that of a land telephone circuit. The operator talks and listens without throwing a switch. He can interrupt the conversation at will, or "break-in". A panel switch knob is provided for turning off the transmitter when listening on the transmitting frequency. Transmitter and receiver are separate units, completely shielded from each other, and each has its own power supply socket. The unit can be installed with individual power supplies for transmitter and receiver, or both may be connected to the same power source. Supply cables should be shielded to prevent

and careful shielding. The receiving antenna and receiver proper are shielded from detector radiation. If complete shielding is desired, supply leads must also be shielded.


The super-regenerative detector is followed by a stage of AF amplification. A volume control is introduced in this circuit, as are ear tip jacks for headphone insertion. The final or output stage employs a power pentode capable of delivering 3.5 watts to the five-inch dynamic speaker which is mounted behind the front panel grill.

### POWER REQUIREMENTS:

250 v.—175 MA (maximum)  
2.5 v.—10.75 amps.

250 v.—175 MA.  
6.3 v.—3.95 amps. (maximum)

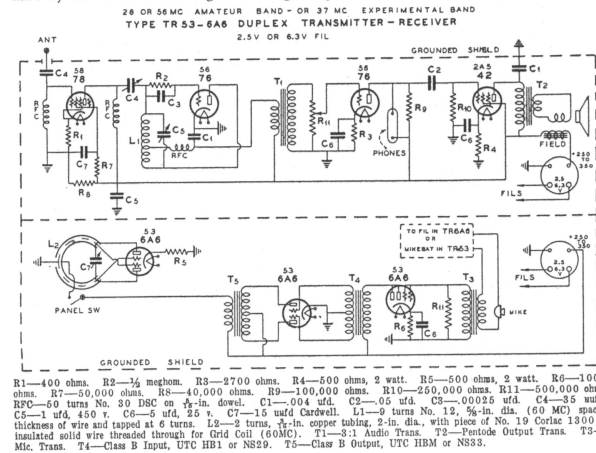Dynamotors running from a six-volt storage battery and delivering 250 v.—175 MA may be used with the TR-53-6A6 for mobile operation.



## A Deaf Mute Asks For An Amateur License—(Continued from page 6)

and also to the federal communication commission to help you get an amateur radio station license."

Station W8LDH of South Haven, Mich., wrote to Adolph to say: "I have showed your letter to various local hams and they all think you should have a license and they will do anything in their power to help you as I will also."

The stack of mail of this nature is legion. All over the country radio hams are writing to Washington to aid the man who refused to be stumped by a disability that would have been insurmountable to many. From coast to coast the night hawks of the air are waiting for the first spoken word of the man who has never spoken and who hopes soon through government generosity to talk direct to his many friends in the crystal whispers of DX. (Adolph Czajka's QSL card is reproduced here.—Ed.)

### FROM ONE SPECIALIST TO ANOTHER

I am the first deaf mute radio fan

I watched ur sigs on my signal recorder white paper tape at.....M., C. S. T. Hrd on.....19.....

Home Made  
100% Signal Recorder Tape  
Tape-puller Power Amplifier  
A pair of 45's Push-Pull  
National's Parts. monitor or  
frequency meter

Believe It or Not  
U C H I'm deaf mute fan as ham  
I hv no head-phone or loud-spr.  
Yy 73 es DX. OM.  
Adolph J. Czajka, Opr.  
(Deaf mute fan as ham)

If you want to read the white paper tape of your sigs  
Write me on ur QSL card OM. I wd send it to u.  
Wud appreciate ur card OM

# - AMATEUR NEWS -

## Largest Amateur Gathering To Be Staged in San Francisco

A TWO-DAY amateur conclave and high-frequency radio show will be staged by the Federation of Radio Clubs of Northern California, a newly-formed association which comprises the more important radio clubs. The purpose of the Federation is to promote better conventions and hamfests and to enable the radio clubs of the entire northern portion of the state to more effectively work together.

New innovations in hamfests are promised when the amateurs of Northern California convene on February 23rd. The affair will close on February 24th. There will be a series of contests to determine the best de-

tions will be answered by a group of more than ten well known technical men.

### PROGRAM

Registration, 9 AM Saturday, February 23rd, 9 to 12 AM, trip to Tropical Beach, Suto Baths.

1 to 5 PM, Technical Round Robin. Chairman, W.G.A.L. Speakers (15 minutes each), Charles Perrine, Jr., W6CUH; Al O'Neil, W6GIS; George Becker; Ralph M. Heinz, W6XBB; Clayton F. Bane, W6WB; Frank C. Jones, W6AJE; John L. Stevens, W6PW; W. W. Smith, W6BCX; J. A. McCullough, W6CHE; Charles Watson, W6DW; J. N. A. Hawkins, W6AAR.

7:30 PM, meeting of delegates of Federated Radio Clubs of Northern California. Visitors welcome.

7:45 PM, political meeting.  
Sunday, February 24th  
9 to 4:2 AM, Hidden 5-meter transmitter hunt and receiver demonstrations in hotel rooms.  
1:30 to 3:30 PM, Two feature speakers.  
3:30 to 5:30 PM, Amateur-built equipment contest.



"The Prize Drawing" — or "After the Raffle Was Over"

signed and constructed pieces of radio equipment; there will be contests for fixed and mobile 5-meter equipment, receiver and transmitter contests. All amateurs are invited to bring their special pieces of equipment. A large number of prizes will be awarded, the total value of which will exceed one thousand dollars. Many of the more valuable prizes will be awarded to those who win the various equipment construction and design contests.

Another of the innovations is the manner in which the prizes will be obtained. The donors of the prizes will be given a pro-rata refund of 75 per cent of the total net receipts. It is hoped that this refund will be ample to reimburse the donors for the actual cost of the prizes.

The registration fee is \$1.50, which includes the banquet ticket. Many of the better prizes will be reserved for those who send in their monies previous to the opening of the conclave.

There will also be a 5-meter hidden transmitter hunt. Many new pieces of equipment will be demonstrated and all of the new receivers will be in action. Hotel rooms have been reserved for the prominent receiver manufacturers. Provisions have been made to install effective antenna systems so that all equipment can be demonstrated to best advantage.

There will be a "round robin" technical meeting. It will be a clearing-house for questions asked by the audience. These ques-

tions will be answered by a group of more than ten well known technical men.

After this, VK6SA in Perth, 2000 miles across Australia, began to come through at good strength and the two VK4's landed him. The chief interest at VK2NO was that just after this, K6EWC's harmonics was heard at QSA4 R4 calling CQ and subsequently working an LU7. This was at 11 AM our time. It was only when K6EWC started working the LU that I realized it was a harmonic. Surely this shows that conditions are becoming favorable for trans-Pacific working again on ten. VK4BB and 4XN had a great day. They worked several VK2's 3's and 6's. This kind of thing hasn't happened since 1928. In December, January and February, a VK-ZL ten-meter contest is running. Here is an opportunity for your ten-meter experiments on the West Coast for us. The contest will be confined to the Sundays, our time, and will run from 8 AM to 8 PM. VK4BB has also heard J2IS on ten, so things are looking up.

All good wishes,  
Don B. Knock,  
Radio Editor, "The Bulletin" (VK2NO-ZNU)

## I. R. F. NEWS

NEW IRF MEMBERS: K7BND, W61TH, W6CSX, W6RHH, W6ICX, W6JWL, W6GV5, VE5EO, and VE5FH. We wish you many IRF QSO's!

● If you know of any YL operators, whom you think can qualify for IRF, we would like to get them listed. It may interest the general membership to know the YL members of IRF to date:

- W7AHJ—Esther Brunk
- VE5KS—May Rose Sparks
- W6EK—Flora Card
- W6DHW—Mac Amarantes
- W5BKV—Sally Walker
- W7NH—Nellie Hart
- W9LW—Lucia Mida
- W6HEG—Harriet Gilbert
- W6AET—Florence Jones

### New Division Chief


● W1BZC, William Ellsworth, has been the Division Chief for the East Coast Division in the past, but has changed his QRA from Massachusetts down to Pennsylvania, and is now in the Capitol Division. Dr. John A. Stewart, W1SK, has very kindly accepted to succeed Mr. Ellsworth in the position of Chief for the East Coast Division. We wish him luck, as they have a fine Division of fine men.

### Eastern News

● W8ELO: "Heartily in favor of east coast gang get-togethers as suggested in last LJ." W2CJP says, "Rehabilitation plan is FB, and it will be the biggest publicity stunt ever pulled for Amateur Radio." His frequency is 5347 KC.
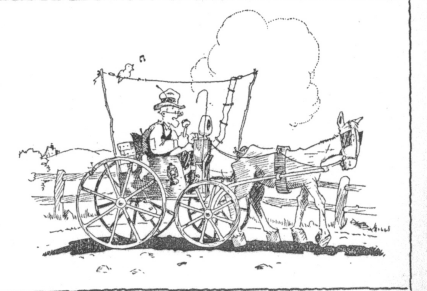
## 5-Meter QRM Problem Solved!

● Farmer "Jinks" and his good horse, "January", have solved the perplexing problem of automobile ignition QRM on 5 meters. If you are troubled with auto noise, or if the 5-meter band in the big cities is overcrowded, do as the good farmer does. The radio inspector will then have an ell of a time finding your QRA.





# A Hum-Free A.C. Operated Pre-Amplifier

By FRANK LESTER\*

• The advantages of all AC operation for high-gain pre-amplifiers intended particularly for condenser and ribbon microphones are so obvious that it is hardly necessary to dilate on them.

In a recent article in an engineering publication, a college professor stated that the requirements for a successful AC pre-amplifier were as follows:

1. Type 57 tubes in triode connection;
2. Heater connections in lead cable on underside of copper chassis;
3. All grid connections above chassis and completely isolated from heater connections;
4. Bias resistors shunted by 25 mf. or larger electrolytic condensers to reduce degeneration on low frequencies;
5. Amplifier completely enclosed

The possible reasons for the hum were listed as follows: 1. Ripple from high voltage power supply; 2. Hum induced in cathode by heater; 3. Inductive pick-up by leads; 4. Inductive pick-up by input and output transformers; 5. Static hum induced in chassis by power transformer.

To determine the extent of 1 and 2, batteries were substituted for the heater and plate supplies, and surprisingly enough the hum dropped only about half. It was evident, then, that problems 3 and 4 would require much investigation.


After attempts to isolate the amplifier from

manner that externally induced E.M.F.s cancel-out in the windings while the primaries continue to induce properly in the secondaries because of their correct phase relationships. As an added measure of protection, the cases of these special transformers were made of special iron having five times the permeability of ordinary stamped sheet iron cases.

When these input and output transformers were installed (batteries still used), the hum dropped to a negligible level, proving conclusively that cause 4, formerly so troublesome, was overcome.


When the AC supply was reconnected to the unit, the hum level came up again, but this time to only about half the level of the first test. Was the hum due to high voltage ripple or cathode modulation by the heater? Juggling of power supplies showed that the heater hum, while appreciable, was small compared to the effect of the rectified plate supply, yet any amount of filter up to 100 mmf. and five or six brute chokes did not reduce the hum and was no better than a simple three-step filter as used in the final amplifier.

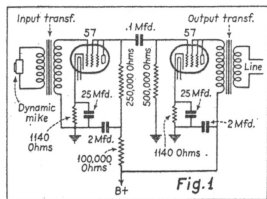It became evident that while the hum was induced by the high voltage supply, it was not due to ripple voltage, and therefore it was static hum of one sort or another. The primary and the high voltage secondary of the power transformer were separated by



Circuit of the experimental set-up

the usual static shield, so it was reasonable to believe that static E.M.F. from the primary would not be impressed on the secondary independently of the straight phenomenon of electromagnetic induction. It was therefore assumed that any form of static E.M.F. in the other windings must come from the high voltage winding, a reasonable assumption because the high voltages developed are high, after all. It might be possible for this winding to induce a static hum in the filament winding, for instance, the hum thus riding into the amplifier by way of the whole filament circuit. There was also a possibility of static E.M.F.s being established in the chassis by this route because of differences of impedances between various grounded points. A similar well-known action takes place in some types of multi-stage RF amplifiers. Even the slightest hum is so aggravat-

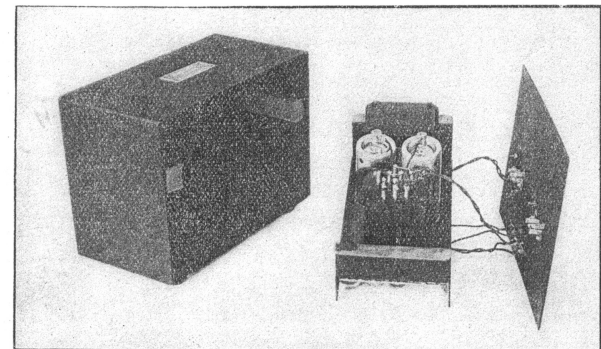

Interior View of Amplifier Case, Showing Soft Rubber Cushion Pads.

in copper case; 6. Completely shielded input connecting to completely shielded microphone; 7. Heater and high voltage supply isolated from amplifier (3 ft. or more) and feeding through shielded cable; 8. Completely filtered high voltage supply.

A unit was built with these features: (1) AC operated; (2) hum free; (3) work with a power amplifier of 70 db gain or more; (4) be capable of raising the level of a velocity mike to at least that of a carbon mike; (5) have a frequency response as flat as possible and preferably at least equal to that of the velocity mike itself.

Even if the first four requirements are met, the last is a problem in itself. Accordingly, the simple circuit of Fig. 1 was selected as a starter and carefully constructed of the best available parts. The 57s were used as triodes, as recommended. An audio oscillator was used for input. The output was coupled through a 200-ohm line to a 15-watt amplifier having a gain of 70 db, the output

of the latter in turn working into a high quality dynamic speaker.

The residual hum produced by the combination was enough to completely overshadow the oscillator input. The conclusion was drawn that a gross error had been made somewhere in the wiring, but repeated checking revealed nothing amiss. The final cures involved some ideas not previously known. All existing wiring by mounting it in a cast, high permeability case 3/4 inch thick, and also shielding all input and both grid and plate leads, it was found that the hum was still too high for practical purposes (battery supply still used). Shielding alone obviously was not sufficient.

As a remedy, hum cancelization right in the transformers themselves was suggested, the shielding of the case alone not being adequate with the amplifier working at the high gain expected of it. Much money was spent on experimental designs, and the final transformers were made with symmetrical primaries and secondaries, poled in such a


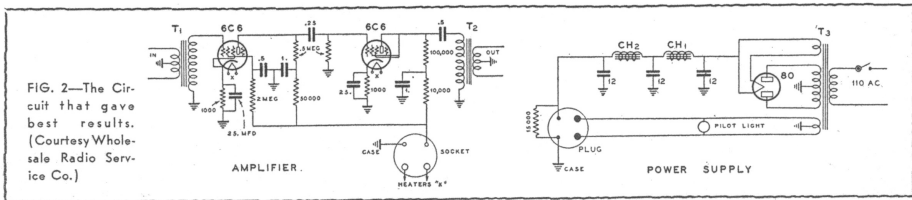


FIG. 2—The Circuit that gave best results. (Courtesy Wholesale Radio Service Co.)

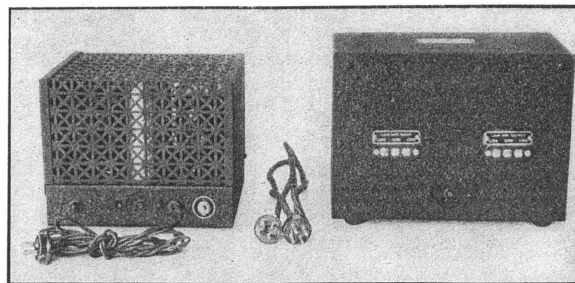


Front and Rear Views of the Amplifier in its Metal Housing.


ing with a high-gain amplifier system that no possibility can be overlooked.

A special transformer was made with all the windings electrostatically shielded from each other. When this transformer was installed, about 90% of the remaining hum disappeared—a most gratifying result.

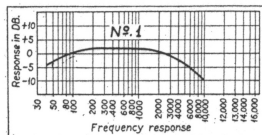
The remaining hum was definitely cathode-heater hum, and its elimination was merely a matter of tube choice. It was found that



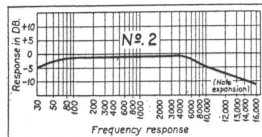
Frequency curve of pre-amplifier with 79 triodes and ordinary transformers.



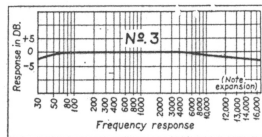Frequency curve of pre-amplifier with 6C6 pentode and 6C6 triode connection, and ordinary transformers.



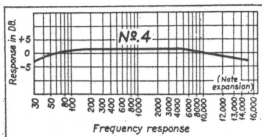Frequency curve of pre-amplifier with special transformers.



Response of entire system illustrated in Fig. 3 and Fig. 4.

6C6s were by far the quietest, the 57 being quite noisy.

With the hum brought down to the point where an experimental pre-amplifier feeding a 15-watt power amplifier was just as quiet with the power switch on or off, the next problem was that of gain, which, after all, is what the amplifier was built for in the first place. The gain must be 40 db or more if a 70 db amplifier is to be driven with sufficient reserve. The circuit of Fig. 1 had only about 38 db gain, which was not enough for a velocity mike. An extra stage did not prove successful because of terrific microphone effects. The final circuit chosen for a commercial wide-range high-fidelity pre-amplifier (Lafayette) is shown in Fig. 2. The first 6C6 is operated as a pentode, the second as a triode. The overall gain was found to be 62 db.


The final problem was frequency response. Curve 1, of an amplifier using the two triodes of a 79 in cascade with good transformers, is shown to illustrate how tube choice can affect amplifier performance. The impedance of the input transformer secondary in this case is about 100,000 ohms. Curve 2 shows the same transformer with a pentode and pentode-triode combination. The reflected input capacity of a triode is influenced by the mutual conductance of the tube; with a pentode it is the actual input capacity as determined by the mere physical construction of the tube.

The practicability of using a pentode first-stage amplifier was a bit of luck, from the standpoint of microphonics as well as frequency response. The high gain makes an intermediate stage unnecessary.

The amplifier response represented by Curve 2 was still not ideal for a high fidelity mike. The possible frequency losses in the amplifier were investigated, and the transformers under ideal conditions were found not to possess the discrepancies shown in the curve. It was also found that a response varying only 1 db from 30 to 17,000 cycles was obtained with the input transformer eliminated and the test input fed directly to the grid circuit of the first amplifier. The input transformer was then held responsible, but since it showed no such loss as mentioned under ideal conditions, the blame was placed on the distributed capacity of the tube, its wiring, etc. To lower the distributed capacity of the transformer secondary, and also to reduce the shunting effect of the tube, the secondary impedance was reduced from 100,000 to 40,000 ohms. The final frequency response as shown in Curve 3 is believed to be as good as anything obtained heretofore.

The gain suffers with reduced secondary impedance, but the final amplification of 56 db (instead of 62 as originally measured) proved altogether sufficient.

As the output transformer is worked at

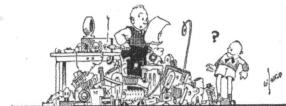


## Ham Hints

—By JAYENAY—
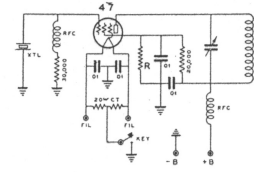
### Eliminating the Chirps When Keying the Crystal

• In the conventional pentode crystal oscillator circuit the screen voltage is obtained from the plate power supply by means of a series dropping resistor. When an attempt is made to key in the center-tap of this crystal oscillator circuit, a bothersome chirp is usually found in the note. When the key is up the screen voltage rises to the same value as the plate voltage, which is from 350 to 450 volts. With the key open, no space current flows through the tube and because there is no current through the screen dropping resistor, there is no voltage drop across that resistor. The high voltage is thus applied to the screen. When the key



R—5000-10,000 OHMS, (TO GET APPROX 100 VOLTS ON SCREEN)

is pressed, and space current starts to flow in the tube, the screen current causes a voltage drop across the usual series dropping resistor and the screen voltage then drops back to its normal 100 volts. However, it does not drop back instantaneously; during the time the screen voltage is dropping there is often a very noticeable change in the frequency, which causes the chirp. The chirp can be eliminated by keeping the screen voltage approximately constant, whether the key is up or down. This necessitates the use of a voltage divider, instead of a series dropping resistor as a source of screen voltage, as shown in the circuit above. The value of the resistance R should be chosen so that the voltage on the screen, when the key is down, is 100 volts when measured with a high resistance voltmeter.

low impedance values, no difficulties with frequency discrimination were experienced with it.

Most of the preceding discussion has been of the electrical features, but the mechanical construction is also of extreme importance. The completed amplifier is shown in the accompanying photographs. Nothing less than 3/8 inch structural steel is used throughout. The pre-amplifier components are mounted on a chassis that slides into sponge rubber guides inside a heavy cabinet measuring 10 3/4 x 7 3/4 x 5 3/8 inches. The front panel, containing the input and output connections and power receptacle, is screwed to the corners of the box, not to the chassis. The latter thus floats perfectly free. The whole unit weighs 25 pounds and nothing short of a deliberate kick affects its microphonically.



## McMURDO-SILVER

### Receiver Prices . . . and Plug-In Coils

Apparently the page of rambling appearing in the December issue of RADIO proved of some interest, to judge from FB cards and comments some of you readers were kind enough to mail in, so here goes for a bit more, mostly on the subject of prices of amateur receivers.

Today there are not one but several good amateur superhets with and without crystal filters available or almost ready below one hundred dollars—in a word at fair prices in terms of design, material and performance. This is as it should be, but the fact that you can now buy a good superhet at a price comparable with good all-wave broadcast receivers—and some of these latter equipped with band spread tuning and beat oscillators are actually better ham receivers than have been available to amateurs as specifically amateur jobs—is largely due to the entry of cost conscious makers into the amateur market.

The point is that amateur receiver design technique has been greatly aided by the all-wave broadcast flurry. So much so that the amateur market looks good today to some of the b.c.l. makers, and in consequence amateur radio is finally getting a break on receiver costs—a break made possible by the cost knowledge of makers who have had to meet serious price competition to live.

The plug-in coil situation is a good example—lots of them cost money—much more money than more convenient, and I believe better, permanently installed coils with a good switching system. And usually in cost lies the hope, if not the actuality, of maker's profit. No, none of us are in business for love alone, although we don't make a nickel net on 5C receivers, though we do have a lot of fun. But if you want to spend over one hundred dollars for a receiver, the dual xtal filter MASTERPIECE III-X is the answer to the super fine receiver question.

And speaking of plug-in coils, there finally seems to be a trend away from them in transmitters—to tapped coils such as the commercials have used for years. This seems quite sensible and I've recently done some checking on the subject of losses in tapped coils in transmitters. The answer was as expected. The losses are measurable, but just measurable, and even if they ran up to 5%, which they don't in a good layout, 5% power isn't much in decibels to the receiving operator when compared to convenience and permanence. Our 10F transmitter is a good example of economy and efficiency—10, 20, 40, 80, or 160 meters by shifting clips on permanently mounted coils. Why not try it in your own rig—you'll be surprised, whether you leave your coils open ended (we prefer it so) or short circuit unused turns. Tnx-cul.

McMurdo Silver

## The MASTERPIECE III-X . . . . . . Is As Revolutionary As the Single Signal

You know what single signal code selectivity is, and of course the MASTERPIECE III-X has this selectivity, although it and the 5C are the only receivers made today that don't sacrifice one iota of sensitivity to get this super-selectivity—you don't lose half an R for its crystal code selectivity. But—it has the new Silver dual crystal circuit that chops out of the air exactly one phone signal at a time, and no more—that eliminates heterodynes within one kc. of the station you want. This is made possible not by the old useless "parallel crystal" scheme that made you wonder what it was ever included in receivers at all for. Not at all! Two crystals 700 cycles apart are used, one alone for code, both in parallel for phone. Thus you get a one kc. wide band, which gets intelligible speech, sans noise, sans heterodynes, sans interference as has never before been possible.

And when you want high quality broadcast, turn the crystal switch and you've got the world's finest broadcast receiver—the receiver that has elicited more enthusiastic praise from experts than all other radios put together have ever received—even good words.



The MASTERPIECE III-X in the opinion of those who have used it in action, is the supreme receiver of all types. For it alone combines without reservation or sacrifice the unequalled and spectacular broadcast performance on all waves of the internationally famous MASTERPIECE III, with the unequalled completeness and flexibility of the 5C, plus the new dual crystal phone selectivity that competitors will begin copying the day they read this ad.

Whatever it is you want, the MASTERPIECE III-X has it. One tuned r.f. stage so good it puts other two-r.f. supers to shame. Three air tuned i.f. stages. Perfect automatic volume control as found in no other receiver in the world—or cut out at the throw of a switch. Separate audio volume and r.f. sensitivity controls. Selectivity anything you want it to be when you want it. Tone quality that out high fidelity's high fidelity. Beauty, ruggedness, ease of operation, band spread anywhere in the range by the originator of "one dial band spread." Briefly, it has every feature found in other sets copied from it by other makers, plus dual crystal filter for real, serious, phone work. Yet it's as low in price as competition that won't even equal the 5C!

### THE 5-C IS TAKING AMATEUR RADIO BY STORM


The 5C is going into more amateur stations today than are practically all other receivers put together! But the answer is simply that it has everything. Name almost any feature you desire and the 5C has it. That's why its predecessor caused W9USA to junk the competitive receivers the World's Fair used in 1933 and get Silver's for 1934. And ask anybody that operated W9USA how they worked!

The 5C is built by a maker who believes in giving, and knows how to give, amateurs full value for their hard earned dollars. It has every feature of sets selling at twice its price, is easy to handle, and has the exclusive and only crystal filter circuit that gives no loss of signal strength in series operation.

This alone would deservedly make it the most popular of amateur receivers and if you don't think it's popular, just ask the QSO's who give you an R9 report what they're using and you'll probably find it's the 5C.

If you want technical dope, it's yours for a postcard—or a look at a back issue of "RADIO" or R/9. But whatever you ask "has it—," the answer is "yes." Tuned r.f., AVC that IS AVC, super-efficient crystal filter, band spread anywhere in its range of 1500 to 23,000 kc., right on the main accurately calibrated, easy to read airplane dial. But why go on—just ask your QSO's! They'll give you the lowdown.

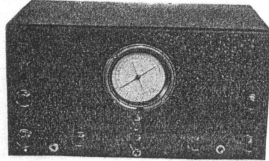Despite all this, the 5C is priced down where it and its competition belong. Just \$74.70 net with Raytheon tubes and Jensen speaker, or \$83.70 complete with specially aligned Xtal filter that is an Xtal filter.



Get it from your jobber, or order direct—you can return it to us within ten days for full refund if you don't think it's a world beater. Oh yes—what other maker dares offer you receivers on such a trial basis?

**McMURDO SILVER, Inc.**  
3362-A NORTH PAULINA STREET CHICAGO, U. S. A.

RADIO FOR JANUARY

### THE 10-F 100 WATT PROFESSIONAL PHONE C-W TRANSMITTER

The type 10F transmitter is the improved and "prettied up" model of the now famous 10D. It is the amateur's dream come true. It provides 100 watts of crystal controlled r.f. power on crystal fundamental in any amateur band, and 60 watts on second crystal harmonic. Its phone carrier output is 25 watts modulated 100% with high fidelity broadcast station modulation, all at a cost below what you can build it for!

It employs one RK-30 screen grid r.f. pentode as a crystal controlled Tritet (electron coupled) oscillator. Modulation is effected by suppressor grid voltage variation, which is obtained from a simple two-stage audio modulator.

But read its specifications, look at its price, and get on the air with 25 watts of broadcast station voice quality or 100 watts C.W. cheaper than you can build a 100 watt telegraph transmitter alone! Order it from your dealer or direct and join the P.W.A.C. Club (Phone Worked All Countries)! If you don't believe it, ask anybody working one. W9NKH has obtained R9 phone reports out of every district—W9DDE sets R9-QSA5 phone out of every district on one installed in Waukegan, Illinois.

#### SPECIFICATIONS

R. F. Output: 100 watts on fundamental crystal frequency. 60 watts on crystal second harmonic. Phone carrier 25 and 15 watts respectively.

Frequency Range: 10, 20, 40, 80 or 160 meter amateur bands. Complete coverage with one set low loss tapped coils included.

Tubes Needed: 1-RK20 Oscillator, 1-RK19 Rectifier, 1-6T Voltage Amplifier, 1-2A5 Power Amplifier, 1-80 Rectifier.

Modulation: Linear suppressor grid modulation variable from zero to over 100% at will. Harmonic distortion less than 5% at 100% modulation.

Audio Frequency Range: Modulation curve flat to 4 db. from 40 to 8000 cycles. Variable tone control provided for high audio frequency attenuation as desired.

A. C. Modulation Hum: Negligible.

Phone-Telegraph Selection: Two position toggle switch on r.f. unit selects phone or C.W. telegraph position at will.

Antenna Tuning: Impedance matching network with two 366 Cardwell mmf. condensers and tapped coil. Will feed any antenna.

Meters: None provided except on special order (mounted on r.f. unit panel). One 0-200 ma. milliammeter and, if desired, one 0-2 antenna thermomometer are all required to check operation.

Controls: Oscillator plate r.f. plate and two antenna tuning dials. Phone-Telegraph, send-receive, modulator on-off and power on-off switches. Screen and plate current measuring and key jacks.


Size: Total height of all three 19x1/8" black crystalline steel reley rack panels 19 1/4". Supplied complete on crystalline black table rack frames.

Power Required: 350 watts at 105 to 125 volts, 50 to 60 cycle A.C.

Accessories Needed: One Billey crystal and holder, one crystal microphone, and tubes as above.

Price Net to Amateurs, \$119.70

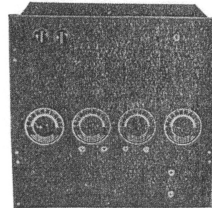Five Raytheon tubes, price \$25.23 net. Turner crystal microphone and cord. Net price to amateurs \$12.60.



# Common Causes of Tube Failure

By LINEAR

• A survey discloses the interesting fact that few amateurs get more than 100 hours of life from their tubes, i.e., the time during which some plate current is flowing—although the filament may be lit for a considerably longer period of time.

Broadcast stations usually expect a minimum tube life of 1000 hours. The tube manufacturer is blamed for most tube failures in amateur stations, especially those of failures that occur in the first few hours of operation. An amateur will take his new 210 or 230A to a dealer for replacement after the tube has been in use for only a few hours. The dealer finds that the amateur has been running the tube at about 50 per cent higher-than-rated plate current. The amateur protests, because another amateur has the same type and make of tube, has used it for two years with the same amount of plate current, and it is still going strong. The manufacturer gets the blame, often unjustly. Few amateurs realize that tubes are most susceptible to failure in the first 15 to 30 hours of operation. Not many of the conventional tubes are "hard" enough to withstand an overload until they have first had an opportunity to harden-up in operation.

Tubes should be "broken in", just like an automobile. For at least 20 hours the tube should be run "lightly" at not much more than about two-thirds of its rated plate current, never at more than the maximum rated plate voltage. The passing of current through the tube actually makes it more free from gas; 99 per cent of tube failures are caused by the presence of gas. A "soft" tube and a "flat" tube generally mean the same thing. "Age" your tubes before attempting to draw maximum plate mills.

A tube that does not turn blue through ionization is regarded as "gas-free" by most amateurs. This indication means nothing at all. Long before there is enough gas present to ionize, the thoriated filament can have its emission materially reduced through thorium poisoning. A thoriated filament requires one of the "hardest" vacuums known to science for satisfactory emission and long life. Tubes with tungsten or oxide-coated nickel filaments can operate satisfactorily in partial vacuums, but these filament materials have other important disadvantages, restricting their use to receiving types or in such tubes where it is impossible to get a really gas-free vacuum, such as in a mercury vapor rectifier or a water-cooled tube. A properly made thoriated filament operating in a truly "hard" vacuum is by far the best all-around filament for transmitting tube use.

For long life it is essential that the tube not only be originally gas-free but that it also remain gas-free throughout its life. This usually means that the plate must not be permitted to show color. In higher-priced tubes, pumped and bombarded during the exhaust period for a relatively long time, it is permissible to operate the tube with some plate color. Even this is dangerous practice because a gas molecule may be released and it will literally go over and bite a big piece out of the filament. The Western Electric tubes with the large molybdenum plates are good examples of a well-pumped tube. Some tubes, of course, are designed for operation with the plate showing color, but these tubes use tantalum as a plate material; the use of nickel is avoided. Usually a hard tube can be identified by the fact that it uses no "getter" to clean-up the tube. The presence of a "getter" is indicated by a splash of silvery coating on a small portion of the inside of the tube.

## Effect of Gas in a Tube

• The deleterious effect of gas in a thoriated tube is caused by the fact that the gas molecule sooner or later breaks up into its constituent atoms, which are then ionized by being struck by a flying electron. This speeding electron, which is traveling on its way from the filament to the plate, strikes the atom of gas and drives one or more electrons out of the atom. Because atoms are neutral, electrically, and because electrons consist of negative particles of electricity, taking one or more electrons out of an atom leaves it with a positive charge. This positively charged remnant of the original atom is called a positive ion and the process of driving electrons out of atoms is called ionization.

The positively charged ion is repulsed by the tremendous positive charge on the plate of the tube and is thus forced in toward the filament. The higher the plate voltage, the higher the velocity of the ion. If the ion is allowed to strike the thoriated tungsten filament, it ruptures the monatomic layer of metallic thorium which covers the surface of the tungsten, and which is the active emitter of electrons. Only a few of these ions are needed to sand-blast the entire active coating of thorium off of the filament. The result is a tube with flat, or low filament emission. However, few of the ions produced by these collisions of electrons and atoms are ever permitted to reach the filament, UNDER NORMAL CONDITIONS.

They are foiled in their dire purpose by what was once considered a deadly enemy—the space charge. The space charge is the cloud of negative electrons which have been thrown off the filament, but which have not yet accelerated away from the filament. An electron thrown off the filament starts out at a relatively low velocity and gradually accelerates until it is traveling at maximum velocity when it reaches the plate. It requires a finite time for the electron to leave the neighborhood of the filament and because it is traveling much faster just before reaching the plate than just after leaving the filament, a cloud of electrons surrounds the filament while relatively few electrons are in the space near the plate. The number of electrons in this space charge cloud depends upon the plate voltage, (leaving the grid out of the discussion for the moment). The higher the plate voltage, the fewer are the electrons in the space charge, because more of them are attracted by the pull of the positive charge on the plate. The cloud of electrons is thickest when there is no plate voltage, and thus no plate current. At high plate currents the cloud is small because it requires a high instantaneous plate voltage to effect the high flow of plate current.

Getting back to the positive gas ion which is speeding in toward the filament, due to the repulsion of the plate, it is seen that the ion exerts an attraction over any loose electron that comes into its field. As soon as it finds an electron it combines with it and turns into an atom again, and thus loses its velocity. This is the process of de-ionization. The atom then wanders around in the tube until another high velocity electron strikes it and ionizes it again. This process is repeated over and over again. The few ions that normally reach the filament in the average tube which is only slightly gassy, do little damage as long as a large space charge surrounds the filament and de-ionizes

all of the gas ions as fast as they appear. However, at high values of plate current the protective sheath of the space charge is greatly impaired and more and more ions are allowed to get through into the filament without being deionized. Thus a gassy tube can have a life of 1000 hours if the plate current is kept down to perhaps 50 per cent of the normal rated plate current, but it may last only one hour more if operated at even its normal rating.

If operated materially above the rated plate current, the filament can fail in a few seconds. Thus if a tube is slightly gassy, the plate current must be held within conservative limits; it will then last for a long period of time. It is much better to have a tube that will last 1000 hours or more, even at reduced plate current, than to squeeze the last possible watt out of it and lay the filament open to the first gas ion that comes along by stealing most of the space charge for the use of the plate circuit.

It should now be evident that an increase in filament voltage to slightly more than the rated voltage will sometimes allow a tube to come back to par. Increasing the filament voltage increases the number of electrons which are thrown off the filament and increases the space charge. If the filament has not been permanently damaged, the thorium coating can be replenished by "boiling" more thorium out of the interior of the tungsten wire which comprises the filament. This "boiling" process is accomplished automatically when the filament voltage is raised.

The average tube engineer designs a tube for a very different purpose than that of amateur operation. He thinks in terms of long life, 24 hour per day operation at perhaps 75 per cent of rated plate current. An examination of the average commercial radio transmitter will show that practically all of the tubes operate at surprisingly low levels, compared with the service that the average amateur demands of the same tube. Thus the tube is designed so that the filament operates at the coolest temperature which permits satisfactory emission. However, such a filament is usually very susceptible to overloads. If the designer were interested in a tube primarily for amateur use at medium and high frequencies, he would first provide an excess of filament and then run it slightly hotter to provide a larger reserve of filament emission in order to increase the effectiveness of the protective space charge sheath previously mentioned.

Thus it is often good practice to increase the filament voltage to about 5 per cent above the rated voltage in order to provide some protection against the occasional overloads to which the average amateur subjects his tubes. This suggestion is aimed particularly at the buyer of new tubes. The precautions should be taken before the damage is done. After the tube begins to turn "flat" it is usually too late to save it. Higher-than-normal filament voltage will undoubtedly shorten the ultimate life of the tube, in some cases as much as 20 per cent. But even a 20 per cent reduction in total life is a small price to pay for insurance against life's darkest moment... when tubes suddenly begin to run hot and become hard to excite. Ultimately they run too cool. The answer? Use a tube that is known to be really hard. Hold the plate current down! Do as the old-timers do... use a transmitter that has sufficient tube capacity so that the filaments are under-loaded rather than overloaded. Another good suggestion is to closely com-

(Continued on page 30)

## Practical High Fidelity

(Continued from page 11)

use with a single or double button microphone, a 200 or 500 ohm line, or a low impedance pickup. In line with the universal nature of the primary winding, the center tapped secondary is designed to operate into push-pull grids or a single grid equally well. In addition to this, a newly developed equalizing structure has been incorporated into this unit. As mentioned above, many radio stations and also many phonograph recordings are not as yet up to true high fidelity standards. Through the use of the tone corrector network incorporated in this transformer structure these can be fully equalized to obtain quality reproduction. The Varitone transformer can also be used to compensate for poor acoustic conditions. This network is not a tone control. Fig. 5 illustrates what can be done to the frequency response of this transformer through the use of the Varitone principle. The curves show what occurs when the control is set at the maximum position when either of the primary windings are working. A is the normal curve of the transformer and this response is obtained when the variable potentiometer arm is set at the center. With B+ strapped to terminal 1 and the potentiometer arm at one end the lows are equalized as in B. With the potentiometer arm at the other end the highs are equalized as in C. If the B+ is strapped to terminal 2 equalization at both ends is obtainable, as in D.

While very great equalization is indicated in these curves, this is controllable from zero to maximum through the Varitone control potentiometer.

The importance of a wide range equalizing transformer for high fidelity radio receiver or PA work cannot be overemphasized. Through the use of controllable equalization veritable "new life" can be given to radio and phonograph music. In addition, this unit affords an inexpensive method of converting an average receiver to high fidelity performance.

It is the writer's impression that high fidelity is here to stay. However, adequate measures should be taken in all high fidelity receivers to allow tone correction for defects in the original program or record fidelity and for the wide range of acoustic conditions of modern homes.

## FOR SALE... GOLD MINE!

A GOLD MINE OF FACTS! Entire volume of 1934 "RADIO", from January to December. Price \$3.00 complete, plus 75¢ postage. Eleven of these volumes on hand. If your order is received too late, your money will be refunded.

"RADIO," Pacific Building, San Francisco, Calif.

**World Famous INTERNATIONAL DX**

3-tube All Electric Short Wave Kit including speaker, 4 coils, 15-200 and diagram.




Wiring extra ..... \$1.75  
Matched Tubes ..... \$2.25  
Broadcast Coil ..... \$ .75  
Cabinet ..... \$1.95

\$6.75

Ask for Circular No. 101  
EXPERIMENTAL RADIO LABS.  
168-R WASHINGTON ST. NEW YORK, N. Y.

# CROWE CABINETS and DIALS

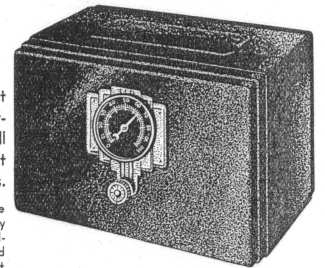

For 5 Meter Transceivers, Short Wave Sets, Monitors, Preselectors, Frequency Meters, Small Portable Transmitters, Test Equipment, and many other uses.


Give your set that finished appearance and necessary protection with a sturdy CROWE cabinet, finished in Crystal-line for permanence and equipped with CROWE tuning control for short wave and other fine tuning.

No. 245 Cabinet for Small 5 Meter Sets

We carry in stock a complete line of name plates, dials, scales, etc., for transmitter panels. Send today for literature illustrating and describing our new material for Amateurs, Experimenters and Set Builders.

Export orders receive special attention, Cable Address—CROWNAME CHICAGO.

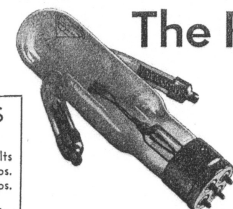**CROWE NAME PLATE & MFG. CO.**  
1755 GRACE STREET CHICAGO, ILL., U. S. A.  
Pacific Coast Representative—W. BERT KNIGHT, INC.



## The RSL-14

### CHARACTERISTICS RSL-14

Filament Potential ..... 2 1/2 volts  
Filament Current ..... 10 Amps.  
Maximum Plate Current 2 Amps.  
Maximum Peak Inverse Potential ..... 10,000 volts

### RSL-9

Filament Potential ..... 2 1/2 volts  
Filament Current ..... 7 Amps.  
Maximum Plate Current ..... 1.2 Amps.  
Maximum Peak Inverse Potential ..... 10,000 volts

... A full-wave rectifier for radio transmission

• This new RSL-14 is a full wave mercury vapor rectifier tube designed for general use in radio transmission. Six outstanding features are:

1. Oxide coated mesh type filament which eliminates peeling of the coating and makes possible large emitting areas capable of supplying electron current greater than required for the plate current.
2. Concentrated filament conserves heat and insures uniform cathode temperature.
3. Two plates in one envelope with one common filament make possible improved regulation and efficiency due to the constant anode cathode potential drop on each half of the cycle.
4. The side arms provide excellent cooling traps for the mercury vapor and keep the vapor pressure down within safe operating range. This design feature prevents arc-backs over a long life.
5. A simple and economical means of mounting the rectifier. Filament terminals are mounted at lower end by means of a .50 watt type tube base. Anode terminals are metal caps at end of arms.
6. The advantage to you in our policy of "Manufacturer to Consumer" is obvious!

RSL-14 ..... \$12.50  
RSL-9 ..... 7.50

## RADIO SCIENTIFIC LABORATORY

410 SO. MARENGO AVENUE ALHAMBRA, CALIF.

You can get the next 4 issues of "RADIO" for \$1.00













Radio Dealers and Jobbers who desire to advertise in these columns are invited to write for rates.

# RADIO BUYERS' GUIDE

A Monthly Listing of Reliable Radio Dealers and Jobbers who solicit the patronage of our readers. Buy from your nearest Dealer or Distributor. He is dependable and reliable.

## CHICAGO, ILLINOIS

Chicago Radio Apparatus Company, Inc.  
415 South Dearborn Street  
Harrison 2276  
Dependable Radio Equipment  
Established 1921

Bulletins on request—we specialize in short wave transmitting and receiving apparatus.  
Catalog Ten cents.

## CHICAGO, ILLINOIS

MID-WEST RADIO MART  
520 South State Street  
CHICAGO

Write for Special Catalog—Free

## CHICAGO, ILLINOIS

Newark Electric Company  
226 W. Madison St.  
Chicago  
All Kinds of Equipment for  
Service Men - Amateurs - Experimenters  
Write for free catalog

## OAKLAND, CALIFORNIA RADIO SUPPLY CO.

2085 BROADWAY.  
Hammarlund, Yaxley, Carter, National, Johnson, IRC, Cardwell, Miller, Morrill, Flechtman, Triplett, Hagis Transceivers  
W6GFY

## ST. PAUL, MINNESOTA

LEW BONN COMPANY  
2484 University Avenue

Rex L. Munger, W9LIP, Sales Engineer  
Radio Wholesaler Complete Stock

## BUFFALO, N. Y.

DYMAC RADIO  
216 E. Genesee St. CL 2080  
Complete Stock Amateur Parts  
STANDARD DISCOUNTS  
—W8AWK—

## LOS ANGELES, CALIFORNIA

RADIO SUPPLY CO.  
912 SO. BROADWAY

The Amateurs' HEADQUARTERS of the WEST


All National Advertised Parts for Receiving and Transmitting carried in stock at all times.

9 Licensed Amateurs on Our Staff


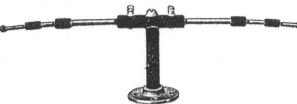
### NEW PRODUCTS

**2 1/2 and Five-Meter Doublet Antenna**  
The new American Radio Hardware Co. 2 1/2 and 5-meter Doublet Antenna is a good solution to the antenna problems encountered in ultra-high frequency transmission and reception. It has always been the desire of the amateur to obtain the maximum efficiency from each piece of equipment used.




Tests conducted within the last few months prove that successful high frequency transmission depends to a great extent on the type of antenna system employed. In most cases, 5 meter antennas were made by the cut and try method and it took hours to "tailor" the antenna for the particular transmitter or receiver. With this new antenna with its special force type locking devices, it is a simple matter to obtain the proper length and this is important—maintain these adjustments for long periods of time.
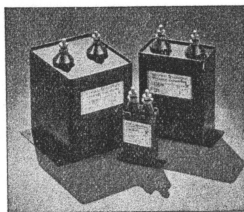
### The New G.E. Pyranol Transmitting Condensers

Inadvertently, the new G.E. Transmitting Condenser cuts were used in this column of the December issue of "RADIO" to describe a group of transmitting condensers manufactured by The Aerovox Corporation. The publishers hasten to correct this error. Here is a description of the new G.E. product, illustrated in the cut below: General Electric D-C Transmitter Capacitors are filled and treated with Pyranol, a nonflammable, non explosive dielectric developed and patented by General Electric. Pyranol has extraordinary insulating and dielectric qualities, and its use makes possible an unusually small and compact unit for all transmitter capacitor ratings. Compare the size with a capacitor of conventional design.

The lacquer-finished cases are hermetically sealed, assuring permanence of the characteristics of the capacitors, as contamination from air and moisture is impossible. Long life and ability to withstand temperatures as high as 75 deg. C. make these capacitors outstanding in their field. Porcelain bushings and mounting feet are included as standard equipment, and the units can be mounted in any position. They are suitable for continuous operation at voltages up to 10 per cent above the rated values.



The New General Electric Pyranol Transmitting Condensers

## CHICAGO, ILLINOIS

Chicago Radio Apparatus Company, Inc.  
415 South Dearborn Street  
Harrison 2276  
Dependable Radio Equipment  
Established 1921

Bulletins on request—we specialize in short wave transmitting and receiving apparatus.  
Catalog Ten cents.

## BUTLER, MISSOURI

HENRY RADIO SHOP  
Complete stock of Collins, Patterson, National, Hammarlund, Silver, Cornell-Dubilier, Thordarson, Sylvania, Taylor, Cardwell, Triplett, Biley, Trimm, Johnson, Turner, and others at lowest wholesale prices. Your used apparatus accepted in trade, too. Write for any information.  
211-215 N. MAIN

## FRESNO, CALIFORNIA

PORTS MANUFACTURING CO.  
3265 E. Belmont Ave. Radio W6AVV  
National FB7-SW3 and Parts; Hammarlund, Cardwell, Biley Crystals; Johnson Insulators. Distributors RCA-DeForest; Transmitting Tubes  
Established 1914 Send for Wholesale Catalog

## SAN FRANCISCO, CALIFORNIA



1452 Market Street.  
"The House of a Million Radio Parts"  
Hammarlund and National sets and parts.  
Sylvania Amateur Transmitting Tubes  
Collins Transmitters.  
Arcturus Receiving Tubes.  
Trimm Phones, all types.  
Johnson Antenna Feeders, Insulators, Transposition Blocks.

## SEATTLE, WASHINGTON



LARGEST PARTS SUPPLY DEPOT IN THE NORTHWEST

Four of Our Employees Are Licensed  
W7BR Amateurs W7CR  
W7AVC W7WE

CORNELL DUBILIER, BLILEY, PATTERSON SETS, COLLINS, WARD, LEONARD, UNITED TRANS.

SCHENECTADY, NEW YORK  
Eastern Radio Supply Company  
712 Broadway

Wholesale Distributors of Tubes, Parts, and Test Equipment for Service Men - Amateurs - Experimenters  
Write for Quotations

... and what SALES VALUE there is in these QUALITY-AT-LOWEST-PRICE Radio Receivers that represent the LAST WORD in Round-the-World reception!

## A model in this group for every purse—American-Foreign and All Wave Radio Receivers

The public is now enthusiastic about radio receivers that will bring in foreign reception. This idea of having world-wide reception is going far to open wide the radio market. For no matter how fine a last year's radio may be—if it does not bring in the foreign stations, the owner is perhaps this moment considering a new radio that will. Certainly he has good

reason for listening when you talk to him about a second set for the home! The market is there... growing every day. Crosley has given you the models to fit every need and every purse. Crosley has given you the program, the goods, and the price. You are losing money if you delay getting in touch with your Crosley distributor.

<p><b>Sixty-One A. F.</b> Eight-tube effectiveness, airplane type dial, automatic volume control, tuning condenser, distinctive cabinet. <b>\$39.95</b></p>	<p><b>614EH 3-Band All Wave</b> Two double purpose tubes provide 8-tube effectiveness. Many distinctive features. Outstanding quality of tone and performance. Low in price. <b>\$49.95</b></p>	<p><b>Seventy-Two A. F.</b> Airplane type dial, automatic volume control, continuous tone control, 10-tube effectiveness. <b>\$59.95</b></p>	<p><b>814FA All Wave</b> Illuminated airplane type dial, dual ratio tuning control, automatic volume control, push-pull output, continuous tone control. Gorgeous cabinet. <b>\$79.50</b></p>
<p><b>Sixty-Four MD (Lowboy)</b> Uses same chassis as Sixty-One A. F. Covers standard broadcasts from 550 to 1700 Kc. and Foreign broadcasts 6,800 to 15,300 Kc. Many distinctive features. <b>\$54.50</b></p>	<p><b>614PS 3-Band All Wave (Lowboy)</b> Uses same chassis as 614EH. Covers standard broadcasts from 540 to 1650 Kc., police, amateur, aviation 1650 to 5000 Kc., Foreign 6800 to 15,300 Kc. <b>\$65.00</b></p>	<p><b>714GA 3-Band All Wave</b> Same cabinet as to left. 3-Band receiver for American-Foreign, police, amateur, aviation reception. <b>\$65.00</b></p>	<p><b>814QB All Wave (Lowboy)</b> An all wave receiver, 630 to 24,000 Kc. Houses same chassis as 814FA. A superbly beautiful cabinet. The ultimate in all wave reception. Attractive in price. <b>\$99.50</b></p>

All prices subject to change without notice. Montana, Wyoming, Colorado, New Mexico and west, prices slightly higher.

**THE CROSLLEY RADIO CORPORATION**  
Home of "the Nation's Station"—WLW—500,000 watts—most powerful in the world—70 on your dial.  
POWEL CROSLLEY, Jr., President CINCINNATI

WHATEVER HAPPENS... YOU'RE THERE WITH A CROSLLEY

# CROSLLEY RADIO